LM3475 Evaluation Board

National Semiconductor Application Note 1381 Wei Gu May 2005



Introduction

The LM3475 evaluation board is provided as a tool for developing DC/DC converters based on the LM3475 IC. As shown in *Figure 1*, the evaluation board is configured to provide an output of 2.5V at up to 2A from an input up to 10V. The corresponding bill of material is given in *Table 1*. Typical efficiencies are shown in *Figure 2* and *Figure 3*. *Figure 4* and *Figure 5* show the board layout.

To aid in the design and evaluation of dc/dc buck converters based on the LM3475 controller, the LM3475 Evaluation Board can be easily re-configured for different output voltages.

Setting Vout

Vout can be set using $\mathsf{R}_{\mathsf{FB1}}$, as shown in the following equation:

$$V_{OUT} = V_{FB} x (R_{FB1} + R_{FB2}) / R_{FB2}$$

Where V_{FB} is 0.8V typically.

Refer to the datasheet before changing any component values, since additional design adjustments may be required.

Optional Components

A feed-forward capacitor C_{FF} is placed on the board, which will increase operating frequency. However, the speed up effect decreases with lower output voltage and is negligible below 1.6V output.

A zero Ohm is used to pull up the EN pin for always on operation. The enable pin can be pulled low at the EN post to shutdown the device. If this resistor is removed, any analog level signal can be used to enable and disable the device.


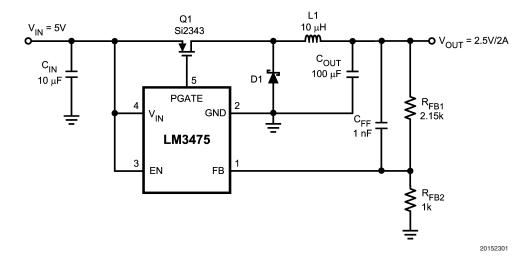


FIGURE 1. Full Demo Board Schematic


AN-1381

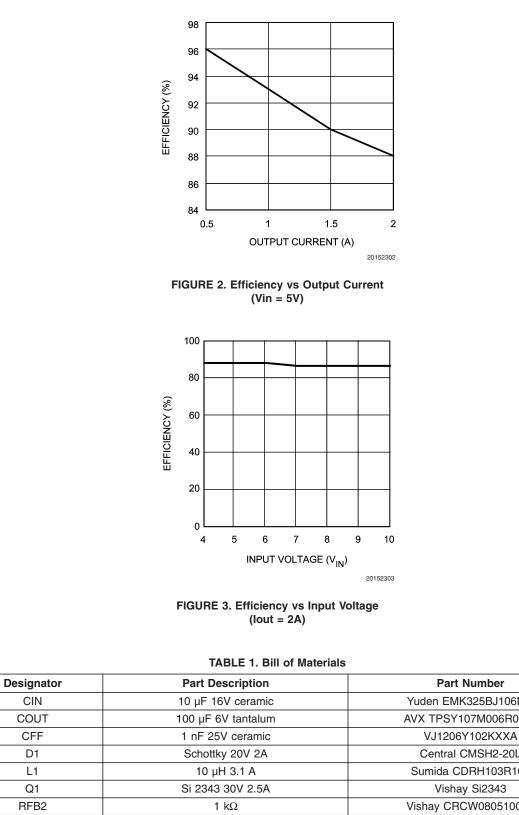

Designator	Part Description	Part Number
CIN	10 µF 16V ceramic	Yuden EMK325BJ106MN
COUT	100 µF 6V tantalum	AVX TPSY107M006R0100
CFF	1 nF 25V ceramic	VJ1206Y102KXXA
D1	Schottky 20V 2A	Central CMSH2-20L
L1	10 µH 3.1 A	Sumida CDRH103R100
Q1	Si 2343 30V 2.5A	Vishay Si2343
RFB2	1 kΩ	Vishay CRCW08051001F
RFB1	2.15 kΩ	Vishay CRCW08052151F
R2	0 Ω	Vishay CRCW08050R00F

www.national.com

PCB Layout Diagram(s)

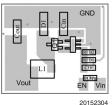

20152304

FIGURE 4. Top Side Layout



20152305

FIGURE 5. Bottom Side Layout

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.



National Semiconductor Americas Customer Support Center Email: new.feedback@nsc.com Tel: 1-800-272-9959

www.national.com

National Semiconductor Europe Customer Support Center Fax: +49 (0) 180-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 69 9508 6208 English Tel: +44 (0) 870 24 0 2171 Français Tel: +33 (0) 1 41 91 8790 National Semiconductor Asia Pacific Customer Support Center Email: ap.support@nsc.com National Semiconductor Japan Customer Support Center Fax: 81-3-5639-7507 Email: jpn.feedback@nsc.com Tel: 81-3-5639-7560