

LM2852X Demonstration Board

National Semiconductor
Application Note 1397
Thatcher Klumpp
September 2005



Introduction

This application note describes the demonstration board for the LM2852X. The LM2852 is a 2A buck regulator belonging to National Semiconductor's SIMPLE SYNCHRONOUS® family. The LM2852 input voltage can range from 2.85V to 5.5V. Output voltages are factory set from 0.8V to 3.3V in 100mV increments. On-chip type-three compensation facilitates simple, low component count power supply design. Two frequency versions of the LM2852 are available: 500 kHz (LM2852Y) and 1500 kHz (LM2852X). The demonstration board for the LM2852X (1500 kHz version) is described in this application note. A separate application note describes the LM2852Y. For detailed information regarding component selection, consult the datasheet.

V_{IN}, GND and V_{OUT}

Three solder terminals are provided for connections to V_{IN}, GND and V_{OUT}. The input voltage to the LM2852 is connected to two PVIN pins and an AVIN pin. PVIN is the supply connected to the output power switches; AVIN powers the controller logic of the regulator. The demonstration board includes filtering of the AVIN voltage using components R_F and C_F. The back side plane of the board is connected to ground through the solder terminal via as well as vias underneath the exposed DAP of the LM2852.

Enable (EN)

The LM2852 enable pin is internally pulled up through a large resistance. The demonstration board includes a via connected to the EN line to facilitate soldering a jumper wire if application of an enable signal is desired.

C_{IN} and C_{INX}

The demonstration board provides two capacitor footprints for the input capacitance. The larger footprint holds the bulk of the capacitance, for example 47 μF. Additional high frequency filtering may also be accomplished by adding a smaller capacitor – C_{INX}. A 1 μF or 100 nF capacitor is commonly used for high frequency filtering.


C_{SS}

The soft-start capacitor is used to control the startup behavior of the switching regulator. A 2.7 nF capacitor yields approximately a 3 ms startup time.

Output Filter - L, and C_O

Since the LM2852 uses on-chip compensation, the output filter component values must be restricted to a certain range. The LM2852X is designed for ceramic output capacitors with ESR values below 10 mΩ. The recommended inductance and capacitance for standard input and output voltages are 1 μH and 10 μF.

Board Schematic

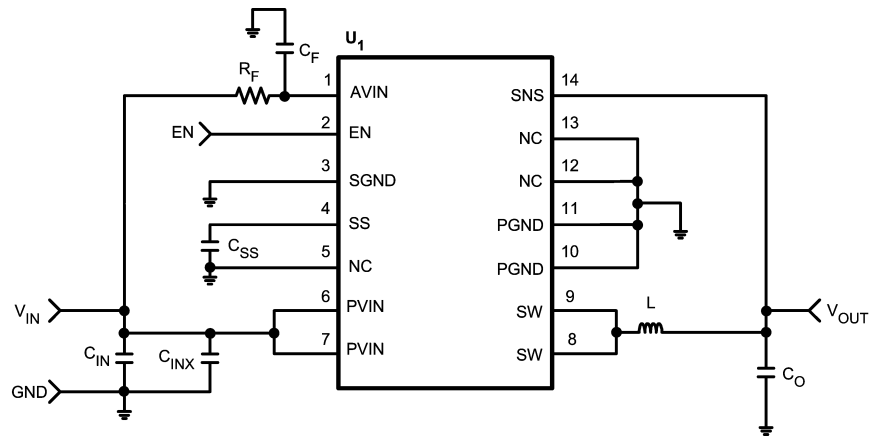


20165401

Bill of Materials for 1500 kHz Solution (LM2852X)


ID	Part Number	Type	Size	Parameters	Qty	Vendor
U ₁	LM2852XMXA-x.x	2A Buck	ETSSOP-14		1	NSC
L	DO1608C-102	Inductor		1 μ H	1	Coilcraft
C _O	GRM31MR61A106KE19	Capacitor	1206	10 μ F/X5R/10V	1	Murata
C _{IN}	GRM31CR60J476M	Capacitor	1206	47 μ F/X5R/6.3V	1	Murata
C _{INX}	GRM188R61A105K	Capacitor	0603	1 μ F/X5R/10V	1	Murata
C _{SS}	VJ0603Y272KXXA	Capacitor	0603	2.7nF \pm 10%	1	Vishay-Vitramon
R _F	CRCW060310R0F	Resistor	0603	10 Ω \pm 10%	1	Vishay-Dale
C _F	GRM188R61A105K	Capacitor	0603	1 μ F/X5R/10V	1	Murata
	160-1026-02-05-00	Solder Terminals		Terminals for VIN, GND and VOUT	3	Wearnes

PCB Layouts: 835 (mil) X 850 (mil)

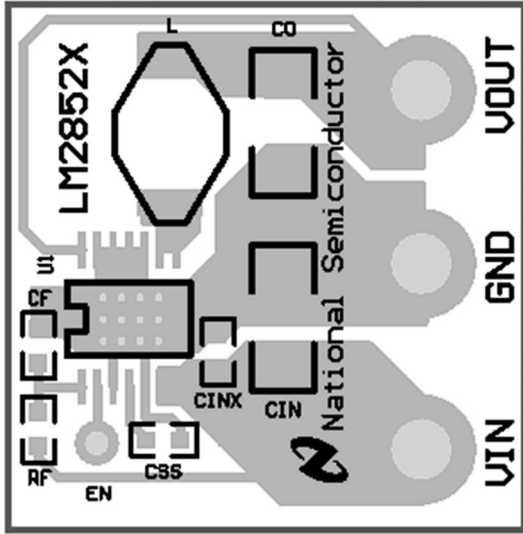

Top Layer


20165402

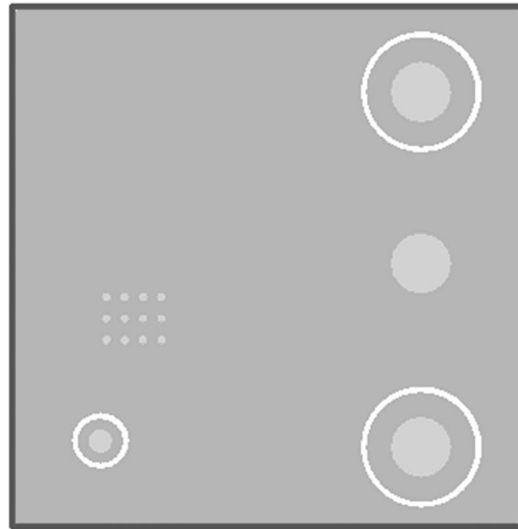

Bottom Layer

20165403

Efficiency Plot

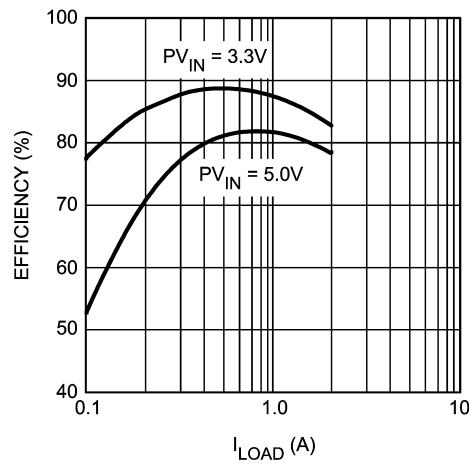

20165404

LM2852X Typical Efficiency for 2.5V Output

Notes

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europa.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560