

LM3205 Evaluation Board

National Semiconductor
Application Note 1413
Haruhiko Yura
January 2006



Introduction

The LM3205 evaluation board is a working demonstration of a step down DC-DC converter. This application note contains information about the evaluation board and board layout considerations. For further information on buck converter topology, device electrical characteristics, and component selection please refer to the LM3205 datasheet.

General Description

The LM3205 is a DC-DC converter optimized for powering RF power amplifiers (RFPAs) from a single Lithium-Ion cell, however the device may be used in many other applications. The LM3205 steps down an input voltage range from 2.7V to 5.5V to a variable output voltage range from 0.8V to 3.6V. Output voltage is set using a V_{CON} analog input for controlling power levels and efficiency of the RFPA.

The LM3205 offers superior performance for mobile phones and similar RFPA applications. Fixed-frequency PWM operation minimizes RF interference. Shutdown function turns the device off and reduces battery consumption to 0.01 μA (typ). The LM3205 is available in a 8-pin lead free micro SMD package. A high switching frequency (2 MHz) allows use of tiny surface-mount components. Only three small external components are required, an inductor and two ceramic capacitors.

Operating Conditions

- V_{IN} range: $2.7\text{V} \leq V_{IN} \leq 5.5\text{V}$
- V_{CON} range: $0.32\text{V} \leq V_{CON} \leq 1.44\text{V}$
- V_{OUT} equation: $V_{OUT} = 2.5 \times V_{CON}$
- I_{OUT} range: $0\text{ mA} \leq I_{OUT} \leq 650\text{ mA}$

Typical Application


 


FIGURE 1. Typical Application Circuit


20169804

Evaluation Board Layout

 

20169808

FIGURE 2. Top Layer

 

20169809

FIGURE 3. Bottom Layer

Connection Diagram and Package Mark Information

 


FIGURE 4.
8-Bump Thin Micro SMD Package, Large Bump
NS Package Number TLA08GNA

Pin Descriptions

Pin #	Name	Description
A1	PV _{IN}	Power Supply Voltage Input to the internal PFET switch.
B1	V _{DD}	Analog Supply Input.
C1	EN	Enable Input. Set this digital input high for normal operation. For shutdown, set low.
C2	V _{CON}	Voltage Control Analog input. V _{CON} controls V _{OUT} in PWM mode.
C3	FB	Feedback Analog Input. Connect to the output at the output filter capacitor.
B3	SGND	Analog and Control Ground
A3	PGND	Power Ground
A2	SW	Switch node connection to the internal PFET switch and NFET synchronous rectifier. Connect to an inductor with a saturation current rating that exceeds the maximum Switch Peak Current Limit specification of the LM3205.

BOM For Common Configurations

	Manufacture	Manufacture #	Description
C1 (input C)	TDK	C2012X5R0J106M	10 μ F, 6.3V, 20%, 0805
C2 (output C)	TDK	C1608X5R0J475M	4.7 μ F, 6.3V, 20%, 0603
C3 (optional, input C)			0.1 μ F, 25V , 0402(Note 1)
C4 (optional, filter for V _{CON})			10 - 100 pF, 25V , 0402(Note 1)
L1 (inductor)	Taiyo-Yuden	NR3015T3R3M	3.3 μ H, 1210mA, 3x3x1.5 mm
R1 (jumper PV _{IN} to V _{DD})	Vishay	CRCW04020R00F	0 Ω , 0402
V _{IN} banana jack - red	Johnson Components	108-0902-001	connector, insulated banana jack (red)
V _{out} banana jack - yellow	Johnson Components	108-0907-001	connector, insulated banana jack (yellow)
GND banana jack - black	Johnson Components	108-0903-001	connector, insulated banana jack (black)

Note 1: C3 and C4 are recommended for a better noise performance.

Board Layout Considerations

 


FIGURE 5. Current Loop

The LM3205 converts higher input voltage to lower output voltage with high efficiency. This is achieved with an inductor-based switching topology. During the first half of the switching cycle, the internal PMOS switch turns on and the input voltage is applied to the inductor in which the current flows from $P_{V_{DD}}$ line to the output capacitor (C2) through the inductor. During the second half cycle, the PMOS turns off and the internal NMOS turns on. The inductor current continues to flow via the inductor from the device PGND line to the output capacitor (C2).

Referring to Figure 5, the LM3205 has two major current loops where pulse and ripple current flow. The loop shown in the left hand side is important because pulse current flows in this path. In the loop on the right hand side, the current waveform in this path is triangular. Pulse current has many high-frequency components due to fast di/dt. Triangular ripple current also has wide high-frequency components. Board layout and circuit pattern design of these two loops are key factors for reducing noise radiation and achieving

stable operation. Other lines, such as input and output terminals are DC current, therefore pattern width (current capability) and DCR drop considerations are needed.

BOARD LAYOUT FLOW

1. Minimize C1, $P_{V_{IN}}$, and PGND loop. These traces should be as wide and short as possible.
2. Minimize L1, C2, SW and PGND loop. These traces also should be as wide and short as possible.
3. The layout patterns should be placed on the component side of the PCB to minimize parasitic inductance and resistance due to via-holes. SW to L1 path should be routed between C2(+) and C2(-) land patterns. If vias are used in these large current paths, multiple via-holes should be used if possible.
4. Connect C1(-), C2(-) and PGND with wide GND pattern. This pattern should be short, so C1(-), C2(-), and PGND are as close as possible. Then connect to a PCB common GND pattern with as many via-holes as possible.
5. SGND should not be connect directly to PGND. Connecting these pins under the device should be avoided. (If possible, connect SGND to the common port of C1(-), C2(-) and PGND.)
6. V_{DD} should not be connected directly to $P_{V_{IN}}$. Connecting these pins under the device should be avoided. It is recommended to connect V_{DD} to the C1(+) to avoid switching noise injection to the V_{DD} line.
7. FB line should be protected from noise. It is recommended to use an inner GND layer (if available) as a shield.

Note: The evaluation board shown in Figure 2 and Figure 3 for the LM3205 was designed with the considerations mentioned above, and it shows good performance. However some aspects have not been optimized because of limitations due to evaluation-specific requirements. The board can be used as a reference. For specific questions, please refer to a National representative.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560