REFERENCE DESIGN

IRAUDAMP10

300W x 2 Channel Class D Audio Power Amplifier Using the IRS2052M and IRF6775

By

Jun Honda, Yasushi Nishimura and Liwei Zheng



CAUTION:

International Rectifier suggests the following guidelines for safe operation and handling of IRAUDAMP10 Demo board;

- Always wear safety glasses whenever operating Demo Board
- Avoid personal contact with exposed metal surfaces when operating Demo Board
- Turn off Demo Board when placing or removing measurement probes

www.irf.com

International **IOR** Rectifier

REFERENCE DESIGN

TABLE OF CONTENTS

TABLE OF CONTENTS	PAGE
INTRODUCTION	3
SPECIFICATIONS	3
CONNECTION SETUP	5
CONNECTOR DESCRIPTION	5
TEST PROCEDURES	6
PERFORMANCE AND TEST GRAPHS	7
SOFT CLIPPING	10
EFFICIENCY	11
THERMAL CONSIDERATIONS	11
THERMAL INTERFACE MATERIAL'S PRESSURE CONTROL	12
POWER SUPPLY REJECTION RATIO (PSRR)	14
SHORT CIRCUIT PROTECTION RESPONSE	15
IRAUDAMP10 OVERVIEW	16
FUNCTIONAL DESCRIPTIONS	
IRS2052M GATE DRIVER IC SELF-OSCILLATING FREQUENCY ADJUSTMENTS OF SELF-OSCILLATING FREQUENCY INTERNAL CLOCK OSCILLATOR SELECTABLE DEAD-TIME	
PROTECTION SYSTEM OVERVIEW	21
CLICK AND POP NOISE REDUCTION	
BUS PUMPING	24
INPUT SIGNAL AND GAIN SETTING	
GAIN SETTING	25
IRAUDAMP10 FABRICATION MATERIALS	
IRAUDAMP10 PCB SPECIFICATIONS	
REVISION CHANGES DESCRIPTIONS	

Introduction

The IRAUDAMP10 Demo board is a reference design which uses only one IC (IRS2052M) to derive appropriate input signals, amplify the audio input, and achieve a two-channel 280 W/ch (4Ω , THD+N=1%) half-bridge Class D audio power amplifier. The reference design demonstrates how to use the IRS2052M Class D audio controller and gate driver IC, implement protection circuits, and design an optimum PCB layout using IRF6775 DirectFET MOSFETs. The reference design contains all the required housekeeping power supplies for ease of use. The two-channel design is scalable, for power and number of channels.

Applications

- AV receivers
- Home theater systems
- Mini component stereos
- Powered speakers
- Sub-woofers
- Musical Instrument amplifiers
- Automotive after market amplifiers

Features

Output Power:	300W x 2 channels (4Ω, THD+N=1%) or 370W x 2 channels (4Ω, THD+N=10%)
Residual Noise:	220μ V, IHF-A weighted, AES-17 filter
Distortion:	0.008% THD+N @ 100W, 4Ω
Efficiency:	90% @ 300W, 4 Ω , single-channel driven, Class D stage
Multiple Protection Features:	Over-current protection (OCP), high side and low side
	Over-voltage protection (OVP),
	Under-voltage protection (UVP), high side and low side
	Over-temperature protection (OTP)
PWM Modulator:	Self-oscillating half-bridge topology with optional clock synchronization

Specifications

General Test Condition	s (unless otherwise noted)	Notes / Conditions
Supply Voltages	±50V	
Load Impedance	4Ω	
Self-Oscillating Frequency	500kHz	No input signal, Adjustable
Gain Setting	30.8dB	1Vrms input yields rated power
Electrical Data	Typical	Notes / Conditions
IR Devices Used	IRS2052M Audio Controller a	nd Gate-Driver,
	IRF6775 DirectFET MOSFET	S
Modulator	Self-oscillating, second order	sigma-delta modulation, analog input
Power Supply Range	± 25V to ±50V	Bipolar power supply
Output Power CH1-2: (1% T	HD+N) 300W	1kHz, ±50V

www.irf.com

IRAUDAMP10 REV 1.1

370W

1kHz, ±50V

Output Power CH1-2: (10% THD+N)

REFERENCE DESIGN

Rated Load Impedance	8-4Ω	Resistive load
Standby Supply Current	+45/-95mA	No input signal
Total Idle Power Consumption	7W	No input signal
Channel Efficiency	90%	Single-channel driven,
		300W, Class D stage


Audio Performance	Class D Output	Notes / Conditions
THD+N, 1W	0.015%	
THD+N, 20W	0.009%	1kHz, Single-channel driven
THD+N, 100W	0.008%	
THD+N, 200W	0.015%	
Dynamic Range	100dB	A-weighted, AES-17 filter, Single-channel operation
Residual Noise, 22Hz - 20kHzAES17	220μV	Self-oscillating – 500kHz
Damping Factor	_51_	1kHz, relative to 4Ω load
Channel Separation	74dB	100Hz
	74dB	1kHz
	70dB	10kHz
Frequency Response : 20Hz-20kHz	±1dB	1W, 4Ω - 8Ω Load
: 20Hz-35kHz	±3dB	100, 432 032 LOUG

Physical Specifications

Dimensions	3.94"(L) x 2.83"(W) x 0.85"(H) 100 mm (L) x 72 mm (W) x 21.5 mm(H)
Weight	0.130kgm

REFERENCE DESIGN

Connection Setup

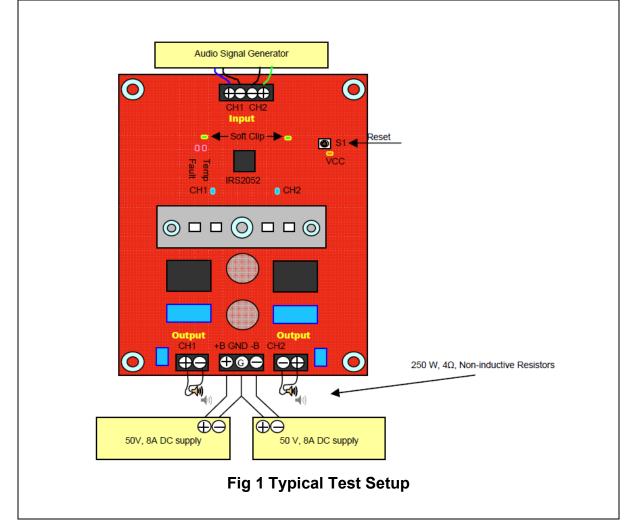

Connector Description

	Pin #	Pin Name	Pin Description		
	1	CH1 INPUT	Analog input for CH1		
CN1	2	GND	Floating ground of Channel 1 input		
CINT	3	GND	Floating ground of Channel 2 input		
	4	CH2 INPUT	Analog input for CH2		
1 -B		-В	-50V supply referenced to GND.		
P1	2	GND	Ground signal from MB.		
3 +B		+B	+50V supply referenced to GND.		
P2	1	CH2 OUTPUT	Output of Channel 2		
P2	2	GND	Floating ground of Channel 2 output		
P3 1 GND Floating ground of Cha		Floating ground of Channel 1 output			
FЭ	2	CH1 OUTPUT	Output of Channel 1		

www.irf.com

Test Procedures

Test Setup:

- 1. Connect 4Ω -200 W dummy loads to 2 output connectors (P2 and P3 as shown on Fig 1) and an Audio Precision analyzer (AP).
- 2. Connect the Audio Signal Generator to CN1 for CH1~CH2 respectively (AP).
- 3. Set up the dual power supply with voltages of ±50V; current limit to 5A.
- 4. TURN OFF the dual power supply before connecting to On of the unit under test (UUT).
- 5. Connect the dual power supply to P1. as shown on Fig 1

Power up:

- 6. Turn ON the dual power supply. The ±B supplies must be applied and removed at the same time.
- 7. One orange and two blue LED should turn ON immediately and stay ON
- 8. Quiescent current for the positive supply should be $45mA \pm 10mA$ at +50V.
- 9. Quiescent current for the negative supply should be $95mA \pm 10mA$ at -50V.

Switching Frequency test

10. With an Oscilloscope, monitor the switching waveform at test points VS1~VS2. Adjust VR1A and VR1B to set the self oscillating frequency to 500 kHz \pm 25 kHz when DUT in free oscillating mode.


Functionality Audio Tests:

- 11. Set the signal generator to 1kHz, 20 mV_{RMS} output.
- 12. Connect the audio signal generator to CN1(Input of CH1,CH2,CH3)
- 13. Sweep the audio signal voltage from 15 mV_{RMS} to 1 $V_{\text{RMS}}.$
- 14. Monitor the output signals at P2/P3 with an oscilloscope. The waveform must be a non distorted sinusoidal signal.
- 15. Observe that a 1 V_{RMS} input generates an output voltage of 34.88 V_{RMS}(CH1/CH2). The ratio, R4x/(R3x) and R30x/(R31x), determines the voltage gain of IRAUDAMP10.

Test Setup using Audio Precision (Ap):

- 16. Use an unbalanced-floating signal from the generator outputs.
- 17. Use balanced inputs taken across output terminals, P2 and P3.
- 18. Connect Ap frame ground to GND at terminal P1.
- 19. Select the AES-17 filter(pull-down menu) for all the testing except frequency response.
- 20. Use a signal voltage sweep range from 15 mV $_{\text{RMS}}$ to 1.5 V $_{\text{RMS}}.$
- 21. Run Ap test programs for all subsequent tests as shown in Fig 2- Fig 7below.


Performance and test graphs

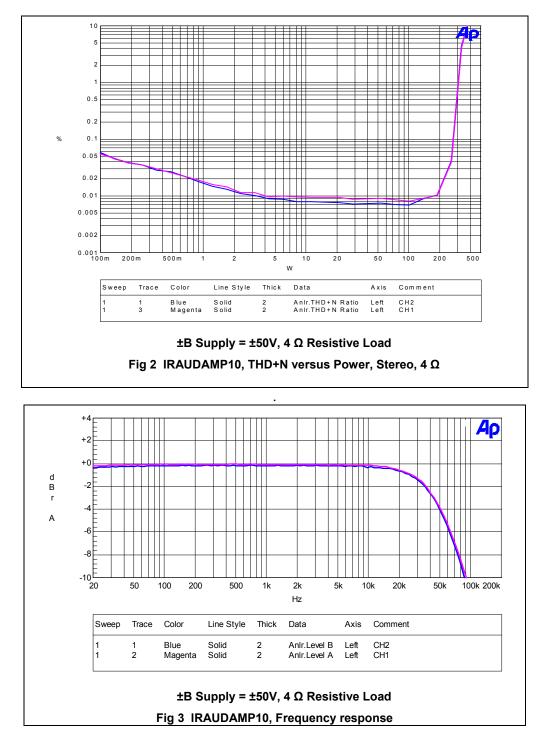


www.irf.com


REFERENCE DESIGN


International

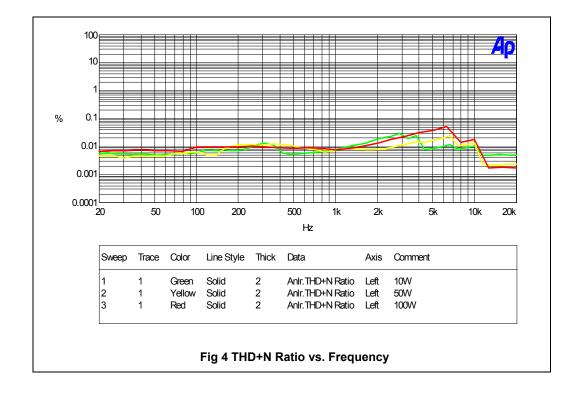

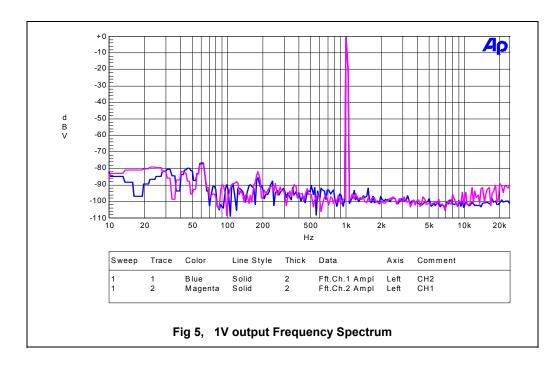


www.irf.com

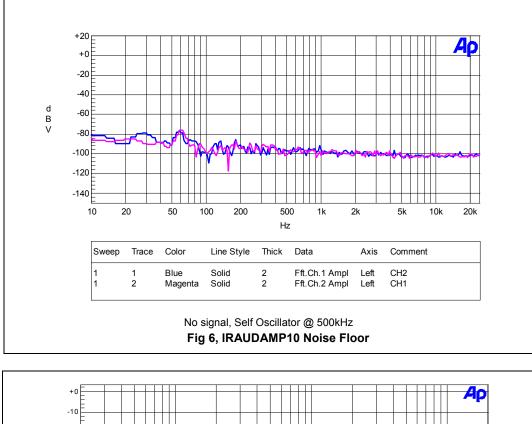

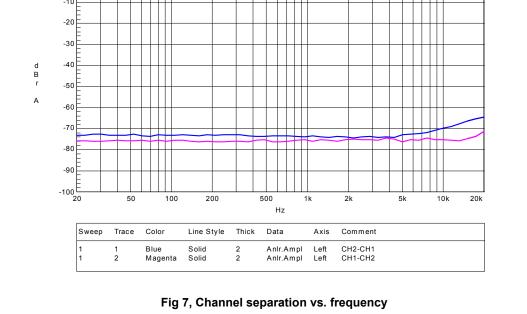

Soft Clipping

IRS2052M has Clipping detection function, it monitors error voltage in COMP pin with a window comparator and pull an open drain nmos referenced to GND. Threshold to detect is at 10% and 90% of VAA-VSS. Each channel has independent CLIP outputs. Once IRS2052M detects Clipping, the CLIP pin can generate pulses to trigger soft clipping circuit, which can limit output's maximum power as Fig 9(soft clipping circuit is not available on AMP10 reference board).

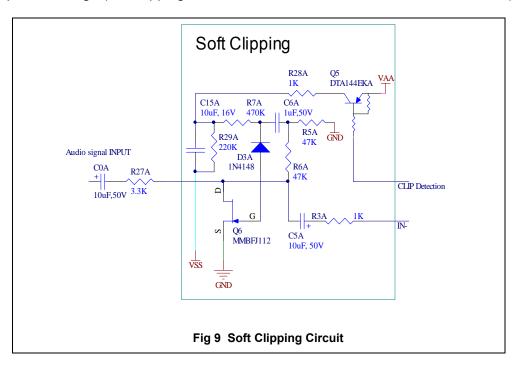


www.irf.com

Efficiency

Fig 10 shows efficiency characteristics of the IRAUDAMP10. The high efficiency is achieved by following major factors:

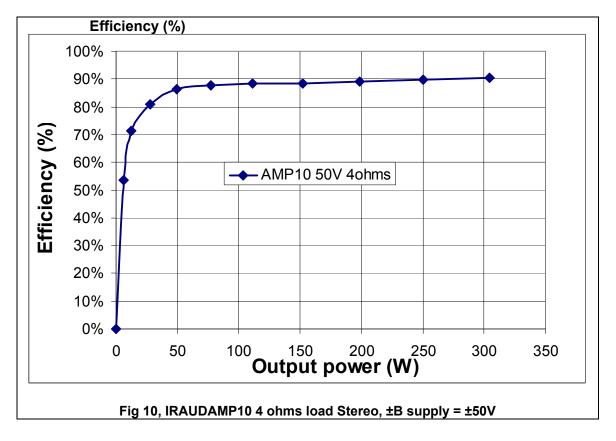- 1) Low conduction loss due to the DirectFETs offering low $R_{DS(ON)}$
- 2) Low switching loss due to the DirectFETs offering low input capacitance for fast rise and fall times

Secure dead-time provided by the IRS2052M, avoiding cross-conduction.



Thermal Considerations

With this high efficiency, the IRAUDAMP10 design can handle one-eighth of the continuous rated power, which is generally considered to be a normal operating condition for safety standards, without additional heatsinks or forced air-cooling.

www.irf.com

Thermal Interface Material's Pressure Control

The pressure between DirectFET & TIM (Thermal Interface Material) is controlled by depth of Heat Spreader's groove. Choose TIM which is recommended by <u>IR</u>. (Refer to AN-1035 for more details). TIM's manufacturer thickness, conductivity, & etc. determine pressure requirement. Below shows selection options recommended:

Mfr.	Material	Туре	Thickness (mils)	Pressure Required	Dispense/ Apply	Clips/ Screws	Can be applied to heat sink?	Mechanical Placement?
Dow Corning	1-4173	1 part heat- cured adhesive	#	Yes	Dispense	Clips	N	Y
Dow Corning	SE 4451	2 part heat- cured adhesive	#	Yes	Dispense	Clips	N	Y
Dow Corning	3-6652	2 part heat- cured adhesive	#	Ves	Dispense	Clips	N	٧
Dow Corning	TP-1500 Pad	Tacky - Phase Change at 52° C	10	>5psi, 20psi typ	Apply	Clips	٧	٧
Bergquist	Gap Pad 3000	conformable filled polymer sheet	15	>10psi	Apply	Clips/ Screws	N	۷
Bergquist	Gap Pad 2000	conformable filled polymer sheet	10	>10psi	Apply	Clips/ Screws	N	Y
Bergquist	Hi Flow 300	Phase Change at 55°C	2.4	>10psi	Apply	Clips	۷	*
Bergquist	Hi Flow 625	Phase Change at 65°C	5	>10psi	Apply	Clips	۷	*
Bergquist	Hi Flow 818	Phase Change at 65°C	5.5	>10psi	Apply	Clips	۷	*
Bergquist	Sil Pad 800	Conformable silicone elastomer	5	>10 higher better	Apply	Clips/ Screws	٧	*
Bergquist	Sil Pad 900	Conformable silicone elastomer	9	>10 higher better	Apply	Clips/ Screws	٧	*
Bergquist	Sil Pad A1500	Conformable silicone elastomer	10	10-50psi	Apply	Clips/ Screws	٧	*
Bergquist	Sil Pad A2000	Conformable silicone elastomer	10	10-50psi	Apply	Clips/ Screws	Y	*
Bergquist	Bond Ply 100	Pressure sensitive adhesive tape	5	>10psi	Apply	Clips	Y	Y
Bergquist	Bond Ply 100	Pressure sensitive adhesive tape	11	>10psi	Apply	Clips	Y	Y
Thermoset (Lord)			#	5-71bf	Dispense	Clips	N	Y
Shin Etsu	X-23- 7783D	Thermal grease	**	-	Dispense	Clips	N	Y
Shin Etsu	X-23- 7762	Thermal grease	##	-	Dispense	Clips	N	Y

Common Thermal Interface Materials Cost Trades

Fig 11 TIM Information


www.irf.com



Check the TIM's compression deflection with constant rate of strain (example as Fig.12) base on manufacturer's datasheet. According to the stress requirement, find strain range for the TIM. Then, calculate heat spreader groove depth as below:


Groove Depth=DirectFET's Height +TIM's Thickness*strain

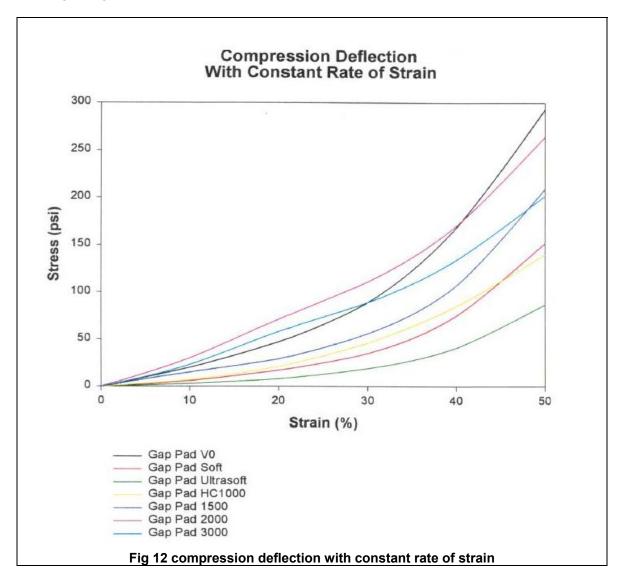**DirectFET's height should be measured from PCB to the top of DirectFET after reflow. The average height of IRF6775 is 0.6mm.



Power Supply Rejection Ratio (PSRR)

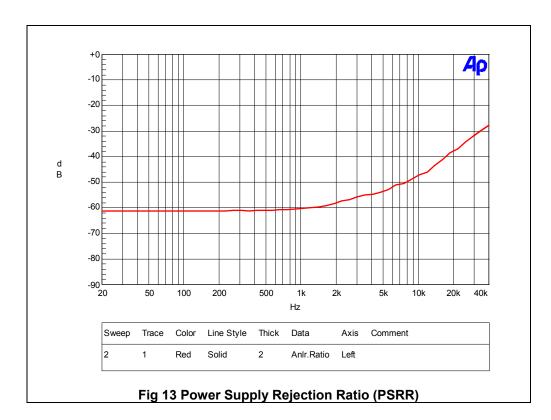
The IRAUDAMP10 obtains good power supply rejection ratio of -60 dB at 1kHz shown in Fig 13. With this high PSRR, IRAUDAMP10 accepts any power supply topology when the supply voltages fit between the min and max range.






Short Circuit Protection Response

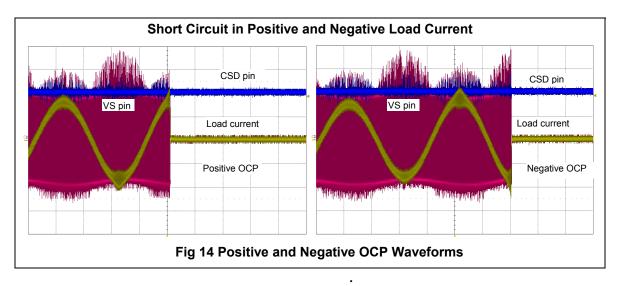Figs 14-15 show over current protection reaction time of the IRAUDAMP10 in a short circuit event. As soon as the IRS2052M detects an over current condition, it shuts down PWM. After one second, the IRS2052M tries to resume the PWM. If the short circuit persists, the IRS2052M repeats try and fail sequences until the short circuit is removed.



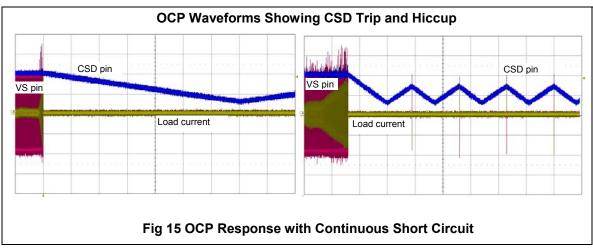



IRAUDAMP10 Overview

The IRAUDAMP10 features a 2CH self-oscillating type PWM modulator for the smallest space, highest performance and robust design. This topology represents an analog version of a second-order sigma-delta modulation having a Class D switching stage inside the loop. The benefit of the sigma-delta modulation, in comparison to the carrier-signal based modulation, is that all the error in the audible frequency range is shifted to the inaudible upper-frequency range by nature of its operation. Also, sigma-delta modulation allows a designer to apply a sufficient amount of error correction.

The IRAUDAMP10 self-oscillating topology consists of following essential functional blocks.

- Front-end integrator
- PWM comparator
- Level shifters
- Gate drivers and MOSFETs
- Output LPF

Integrator

Referring to Fig 16 below, the input operational amplifier of the IRS2052M forms a front-end second-order integrator with R3x, C2x, C3x, and R2x. The integrator that receives a rectangular feedback signal from the PWM output via R4x and audio input signal via R3x generates a quadratic carrier signal at the COMP pin. The analog input signal shifts the average value of the quadratic waveform such that the duty cycle varies according to the instantaneous voltage of the analog input signal.

PWM Comparator

The carrier signal at the COMP pin is converted to a PWM signal by an internal comparator that has a threshold at middle point between VAA and VSS. The comparator has no hysteresis in its input threshold.

Level Shifters

The internal input level-shifter transfers the PWM signal down to the low-side gate driver section. The gate driver section has another level-shifter that level shifts up the high-side gate signal to the high-side gate driver section.

www.irf.com




Gate Drivers and DirectFETs

The received PWM signal is sent to the dead-time generation block where a programmable amount of dead time is added into the PWM signal between the two gate output signals of LO and HO to prevent potential cross conduction across the output power DirectFETs. The high-side level-shifter shifts up the high-side gate drive signal out of the dead-time block.

Each channel of the IRS2052M's drives two DirectFETs, high- and low-sides, in the power stage providing the amplified PWM waveform.

Output LPF

The amplified PWM output is reconstructed back to an analog signal by the output LC LPF. Demodulation LC low-pass filter (LPF) formed by L1 and C13, filters out the Class D switching carrier signal leaving the audio output at the speaker load. A single stage output filter can be used with switching frequencies of 500 kHz and greater; a design with a lower switching frequency may require an additional stage of LPF.

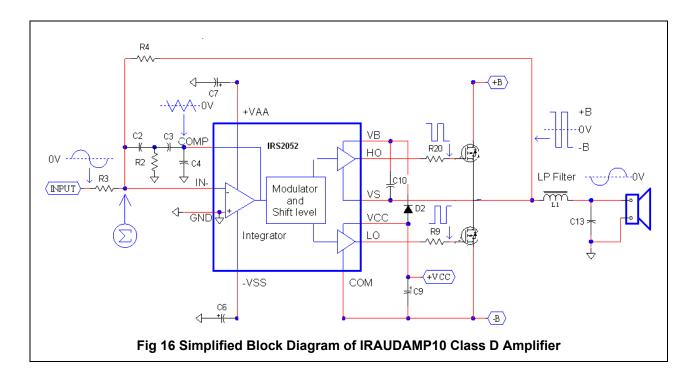

www.irf.com


Functional Descriptions

IRS2052M Gate Driver IC

The IRAUDAMP10 uses the IRS2052M, a 2 Channel high-voltage (up to 200 V), high-speed power MOSFET driver with internal dead-time and protection functions specifically designed for Class D audio amplifier applications. These functions include OCP and UVP. The IRS2052M integrates bi-directional over current protection for both high-side and low-side MOSFETs. The dead-time can be selected for optimized performance according to the size of the MOSFET, minimizing dead-time while preventing shoot-through. As a result, there is no gate-timing adjustment required externally. Selectable dead-time through the DT pin voltage is an easy and reliable function which requires only two external resistors, R12 and R13 as shown on Fig 17 or Fig 23 below.

The IRS2052M offers the following functions.

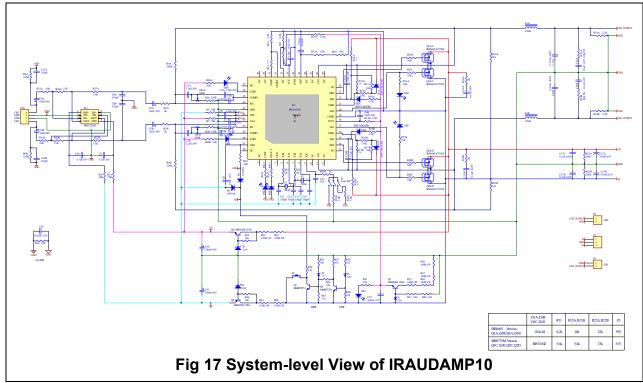- PWM modulator
- Dead-time insertion
- Over current protection
- Under voltage protection
- Level shifters



Refer to IRS2052M datasheet and AN-1159 for more details.

www.irf.com



Self-Oscillating Frequency

Self-oscillating frequency is determined by the total delay time along the control loop of the system; the propagation delay of the IRS2052M, the DirectFETs switching speed, the time-constant of front-end integrator (R2x, R3x, R4x, Vr1x, C2x, C3x). Variations in +B and –B supply voltages also affect the self-oscillating frequency.

The self-oscillating frequency changes with the duty ratio. The frequency is highest at idling. It drops as duty cycle varies away from 50%.

Adjustments of Self-Oscillating Frequency

Use VR1x to set different self-oscillating frequencies. The PWM switching frequency in this type of self-oscillating switching scheme greatly impacts the audio performance, both in absolute frequency and frequency relative to the other channels. In absolute terms, at higher frequencies, distortion due to switching-time becomes significant, while at lower frequencies, the bandwidth of the amplifier suffers. In relative terms, interference between channels is most significant if the relative frequency difference is within the audible range.

Normally, when adjusting the self-oscillating frequency of the different channels, it is suggested to either match the frequencies accurately, or have them separated by at least 25kHz. Under the normal operating condition with no audio input signal, the switching-frequency is set around 500kHz in the IRAUDAMP10.

Internal Clock Oscillator

The IRS2052M integrates two clock oscillators and synchronization networks for each PWM channel. To prevent AM radio reception interference, two PWM frequencies are selectable via XSL pin. As shown in Table 2, when XSL is bias to VAA, X1A and X1B are active. When XSL is GND X2A and X2B are active. When XSL is VSS, both clock oscillators are disabled.


XSL pin X1A/B		X2A/B
VAA	Activated	Disabled
GND Disabled		Activated
VSS	Disabled	Disabled

CKO outputs internal clock with VAA/VSS amplitude. The CKO can distribute clock signal to multiple IRS2052 devices to synchronize PWM switching timing.

www.irf.com

Selectable Dead-time

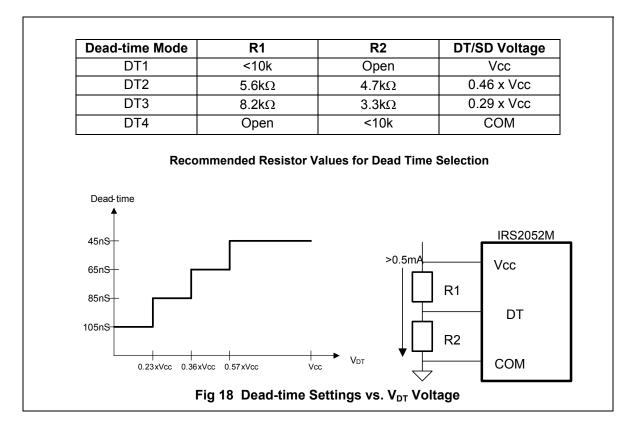The dead-time of the IRS2052 is set based on the voltage applied to the DT pin. Fig 18 lists the suggested component value for each programmable dead-time between 45 and 105 ns. All the IRAUDAMP10 models use DT1 (45ns) dead-time.






Protection System Overview

The IRS2052M integrates over current protection (OCP) inside the IC. The rest of the protections, such as over-voltage protection (OVP), under-voltage protection (UVP), and over temperature protection (OTP), are detected externally to the IRS2052M (Fig 19).

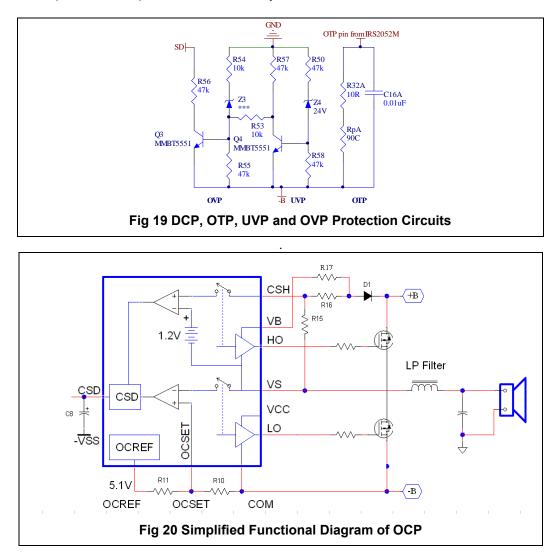The external shutdown circuit will disable the output by pulling down CSD pins, (Fig 20). If the fault condition persists, the protection circuit stays in shutdown until the fault is removed.



www.irf.com



Over-Current Protection (OCP)

Low-Side Current Sensing

The low-side current sensing feature protects the low side DirectFET from an overload condition from negative load current by measuring drain-to-source voltage across $R_{DS(ON)}$ during its on state. OCP shuts down the switching operation if the drain-to-source voltage exceeds a preset trip level.

The voltage setting on the OCSET pin programs the threshold for low-side over-current sensing. When the VS voltage becomes higher than the OCSET voltage during low-side conduction, the IRS2052 turns the outputs off and pulls CSD down to -VSS.

High-Side Current Sensing

The high-side current sensing protects the high side DirectFET from an overload condition from positive load current by measuring drain-to-source voltage across $R_{DS(ON)}$ during its on state. OCP shuts down the switching operation if the drain-to-source voltage exceeds a preset trip level.

High-side over-current sensing monitors drain-to-source voltage of the high-side DirectFET during the on state through the CSH and VS pins. The CSH pin detects the drain voltage with reference to the VS pin, which is the source of the high-side DirectFET. In contrast to the low-side current sensing, the threshold of the CSH pin to trigger OC protection is internally fixed at 1.2V. An external resistive divider R15, R16 and R17 are used to program a threshold as shown in Fig 20. An external reverse blocking diode D1 is required to block high voltage feeding into the CSH pin during low-side conduction. By subtracting a forward voltage drop of 0.6V at D1, the minimum threshold which can be set for the high-side is 0.6V across the drain-to-source.

Over-Voltage Protection (OVP)

OVP is provided externally to the IRS2052M. OVP shuts down the amplifier if the bus voltage between GND and -B exceeds 51V. The threshold is determined by a Zener diode Z3. OVP protects the board from harmful excessive supply voltages, such as due to bus pumping at very low frequency-continuous output in stereo mode.

Under-Voltage Protection (UVP)

UVP is provided externally to the IRS2052M. UVP prevents unwanted audible noise output from unstable PWM operation during power up and down. UVP shuts down the amplifier if the bus voltage between GND and -B falls below a voltage set by Zener diode Z4.

Offset Null (DC Offset) Adjustment

The IRAUDAMP10 requires no output-offset adjustment. DC offsets are tested to be less than ±20 mV.

www.irf.com

Over-Temperature Protection (OTP)

The over temperature protection input OTP is for an external PTC Thermistor to monitor temperature of MOSFET. The OTP pin equips a 0.6mA internal current source to bias the external PTC resistor. Over temperature warning activates when the voltage at any of OTP input pin goes higher than 1.4V. Over temperature protection activates when the voltage at any of OTP input pin goes higher than 2.8V. A PTC thermistors, Rpa in Fig 19, is placed on bottom side PCB; which is close to the 4 DirectFETs; and monitors DirectFETs' temperature. If the temperature rises above 90 °C on the bottom side, make OTP input pin goes high and shuts down all 2 channels by pulling down the CSD pins of the IRS2052M. OTP recovers once the temperature cools down.

On-chip Over Temperature Protection

If the junction temperature TJ of IRS2052M becomes higher than on-chip thermal warning threshold 127°C, the on-chip over temperature protection pulls OTW pin down to GND. If the junction temperature TJ keeps increasing and exceed on-chip thermal shutdown threshold 147°C, the on-chip over temperature protection shuts down PWM, pulls OTW up to VAA and pulls FAULT pin down to GND as long as the junction temperature is higher than the threshold.

Over Temperature Warning Output (OTW)

OTW output is an open drain output referenced to GND to report whether the IRS2052M is experiencing high temperature from either OTP input or on-chip OTP. OTW activates if OTP pin voltage becomes higher than warning threshold, or if junction temperature reaches warning threshold.

Fault Output

FAULT output is an open drain output referenced to GND to report whether the IRS2052M is in shutdown mode or in normal operating condition. If FAULT pin is open, the IRS2052M is in normal operation mode.

Following conditions triggers shutdown internally and pulls FAULT pin down to GND.

- Over Current Protection
- Over Temperature Protection (internal or external via OTP pin)
- Shutdown mode from CSD pin voltage

Click and POP Noise Reduction

Thanks to the click and pop elimination function built into the IRS2052M, the IRAUDAMP10 does not require any additional components for this function.

www.irf.com



Power Supply Requirements

For convenience, the IRAUDAMP10 has all the necessary housekeeping power supplies onboard and only requires a pair of symmetric power supplies.

House Keeping Power Supply

The internally-generated housekeeping power supplies include ±5V for analog signal processing, and +12V supply (V_{CC}) referred to the negative supply rail -B for DirectFET gate drive. The gate driver section of the IRS2052M uses VCC to drive gates of the DirectFETs. V_{CC} is referenced to – B (negative power supply). D2x, R18x and C10x form a bootstrap floating supply for the HO gate driver.

Bus Pumping

When the IRAUDAMP10 is running in stereo mode, the bus pumping effect takes place with low frequency, high output. Since the energy flowing in the Class D switching stage is bi-directional, there is a period where the Class D amplifier feeds energy back to the power supply. The majority of the energy flowing back to the supply is from the energy stored in the inductor in the output LPF. Usually, the power supply has no way to absorb the energy coming back from the load. Consequently the bus voltage is pumped up, creating bus voltage fluctuations.

Following conditions make bus pumping worse:

- 1. Lower output frequencies (bus-pumping duration is longer per half cycle)
- 2. Higher power output voltage and/or lower load impedance (more energy transfers between supplies)
- 3. Smaller bus capacitance (the same energy will cause a larger voltage increase)

The OVP protects IRAUDAMP10 from failure in case of excessive bus pumping. Bus voltage detection monitors only +B supply, assuming the bus pumping on the supplies is symmetric in +B and -B supplies.

Load Impedance


Each channel is optimized for a 4 Ω speaker load in half bridge.

Input Signal and Gain Setting

A proper input signal is an analog signal ranging from 20Hz to 20kHz with up to 3 V_{RMS} amplitude with a source impedance of no more than 600 Ω . Input signal with frequencies from 30kHz to 60kHz may cause LC resonance in the output LPF, causing a large reactive current flowing through the switching stage, especially with greater than 8 Ω load impedances, and the LC resonance can activate OCP.


www.irf.com

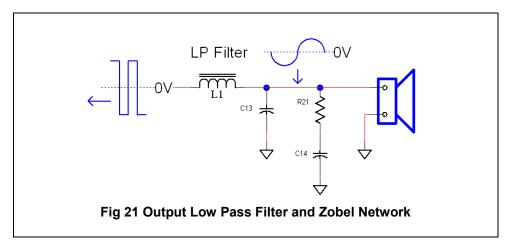The IRAUDAMP10 has an RC network called a Zobel network (R21 and C14) to damp the resonance and prevent peaking frequency response with light loading impedance. (Fig 21)



Gain Setting

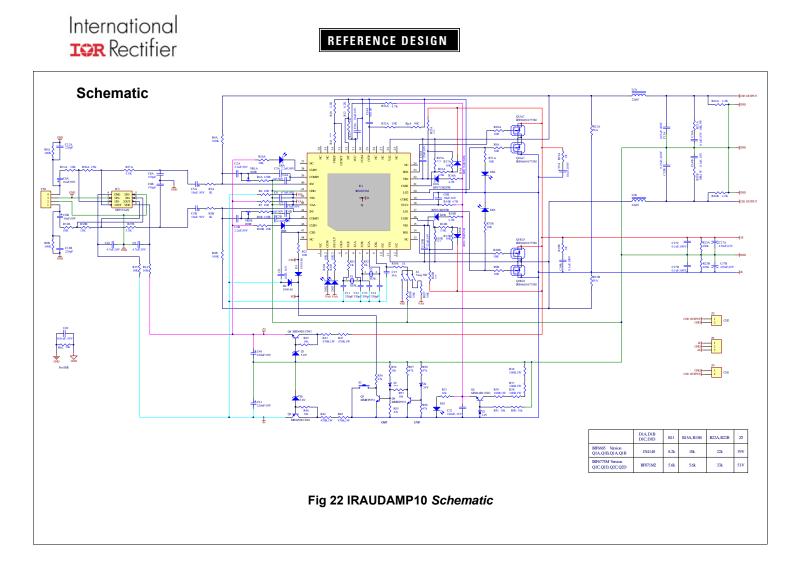The ratio of resistors {R4x/(R3x+R27x)}*(R30x/R31x) in Fig 22 sets voltage gain. The IRAUDAMP10 has no on board volume control. To change the voltage gain, change the input resistor term R27x and R3x. Changing R4x affects PWM control loop design and may result poor audio performance.



www.irf.com

IRAUDAMP10 REV 1.1

Page 26 of 34

IRAUDAMP10 Fabrication Materials

Table 1 IRAUDAMP10 Electrical Bill of Materials

Quantity	Value	Description	Designator	Part Number	Vender
4	10uF, 50V	CAP 10UF 50V ELECT SMG RAD	C0A, C0B, C5A, C5B	565-1106-ND	United Chemi-Con
		CAP CER 2200PF 50V 10%			Murata Electronics
4	2.2nF,50V	X7R 0603 CAP 1000PF 50V	C2A, C2B, C3A, C3B	490-1500-1-ND	North America
2	1nF,50V	CERAMICX7R 0603	C4A, C4B	399-1082-1-ND	Kemet
4	4.7uF,10V	CAP CERM 4.7UF 10V Y5V 0805	C6, C7, C9, C10	478-1429-1-ND	AVX Corporation
1	10uF, 16V	CAP CER 10UF 16V Y5V 1206	C8	490-3383-1-ND	Murata Electronics North America
		Polypropylene Film			
2	470pF	Capacitors 100V 470pF 5% CAP CER 10UF 16V Y5V	C8A, C8B	505-FKP2470/100/5	WIMA Murata Electronics
2	10uF,16V	0805	С9А, С9В	490-3347-1-ND	North America
2	22uF,16V	CAP CER 22UF 16V X7R 1210	C10A, C10B	445-3945-1-ND	TDK Corporation
4	330pF, 50V	CAP CER 330PF 50V X7R 0603	C11, C12, C13, C14	445-5074-1-ND	TDK Corporation
	550pi , 50V	CAP CER 220PF 50V 10%		443-3074-1-110	Murata Electronics
2	220pF	X7R 0603 CAP .47UF 400V METAL	C12A, C12B	490-1483-1-ND	North America
2	0.47uF, 400V	POLYPRO	C13A, C13B	495-1315-ND	EPCOS Inc
2	0.1uF, 63V	CAP FILM MKP .1UF 63VDC 2%	C14A, C14B	BC2054-ND	Vishay/BC Components
		CAP CER 10000PF 50V 10%			Murata Electronics
2	0.01uF,50V	X7R 0603 CAP 470UF 63V ELECT	C16A, C62	490-1512-1-ND	North America
2	470uF,63V	SMG RAD	C17A, C17B	565-1131-ND	United Chemi-Con
4	0.1uF,100V	CAP CER .10UF 100V X7R 10% 0805	C17C, C17D, C19A, C19B	445-1418-1-ND	TDK Corporation
1	100uF, 25V	CAP 100UF 25V ELECT SMG RAD	C32	565-1059-ND	United Chemi-Con
2	220uF, 10V	CAP 220UF 10V ELECT SMG RAD	C40, C41	565-1021-ND	United Chemi-Con
		TERMINAL BLOCK 3.5MM			On Shore Technology
1	INPUT	4POS PCB	CN1	ED1516-ND	Inc
4	RF071M2STR	DIODE 200V 700MA SOD123 DIODE SWITCH 100V	D1A, D1B, D2A, D2B	RF071M2SCT-ND	Rohm Semiconductor
2	1N4148	400MW SOD123	D3, D4	1N4148W-FDICT-ND	Diodes Inc
1	LED AMBER	LED AMBER CLR THIN 0805 SMD	DS1	160-1419-1-ND	Lite-On Inc
2	LED RED	LED SUPER RED CLEAR 0805 SMD	DS2, DS3	160-1415-1-ND	Lite-On Inc
2	LED BLUE	LED 468NM BLUE CLEAR 0805 SMD	DS4, DS5	160-1645-1-ND	Lite-On Inc
		LED GREEN CLEAR 0805			
2 1	LED GREEN IRS2052M	SMD 2ch Audio Class D Controller	DSA, DSB IC1	160-1414-1-ND IR2052MPBF	Lite-On Inc International Rectifier
		IC OPAMP DUAL LOW			
1	NE5532AN	NOISE 8-DIP	IC3	NE5532ANGOS-ND	ON Semiconductor Inductors,Inc./SAGAMI
2	22uH	Class D inductor, 22uH CONN TERM BLOCK PCB	L1A, L1B	7G17A-220M	ELEC CO., LTD.
1	Header 3	5.0MM 3POS	P1	281-1415-ND	Weidmuller
2	SP OUT	CONN TERM BLOCK PCB 5.0MM 2POS	P2, P3	281-1414-ND	Weidmuller
2	MJD44H11T4G	TRANS PWR NPN 8A 80V DPAK	Q1, Q8	MJD44H11T4GOSCT- ND	ON Semiconductor
£		MOSFET, 150V, 28A, 47			
4	IRF6775MPBF	mOhm, 25 nC Qg, Med Can, optimized for Audio	Q1A, Q1B, Q2A, Q2B	IRF6775MTR1PBF	International Rectifier

www.irf.com

REFERENCE DESIGN

		MOSFET, 100V, 19A, 62			
		mOhm, 8.7 nC Qg, Small			
0	N/A	Can, optimized for Audio	Q1C, Q1D, Q2C, Q2D	IRF6665TR1PBF	International Rectifier
-		TRANS NPN 160V 350MW		MMBT5551-FDICT-	
2	MMBT5551	SMD SOT23-3	Q3, Q4	ND	Diodes Inc
		TRANS PWR PNP 8A 80V		MJD45H11T4GOSCT-	
1	MJD45H11T4G	DPAK	Q9	ND	ON Semiconductor
		RES 100K OHM 1/10W 5%			
4	100K	0603 SMD	R0A, R0B, R23A, R23B	RHM100KGCT-ND	Rohm Semiconductor
		RES 120 OHM 1/10W 5%			
2	120R	0603 SMD	R2A, R2B	RHM120GCT-ND	Rohm Semiconductor
	414	RES 1.00K OHM 1/8W 1%			
2	1K	0805 SMD	R3A, R3B	RHM1.00KCRCT-ND	Rohm Semiconductor
2	100K	RES 100K OHM 1/8W 1% 0805 SMD	R4A, R4B	RHM100KCRCT-ND	Rohm Semiconductor
2	IUUK	0805 3100	R6, R7, R9A, R9B, R14,	RHM100KCRC1-ND	Romm Semiconductor
		RES 10 OHM 1/10W 5%	R15, R20A, R20B, R22,		
10	10R	0603 SMD	R32A	RHM10GCT-ND	Rohm Semiconductor
10		RES 2.2K OHM 1/10W 5%			
1	2.2K	0603 SMD	R10	RHM2.2KGCT-ND	Rohm Semiconductor
		RES 5.6K OHM 1/10W 5%			
3	5.6K	0603 SMD	R11, R15A, R15B	RHM5.6KGCT-ND	Rohm Semiconductor
		RES 8.2K OHM 1/10W 5%			· · · · · · ·
1	8.2K	0603 SMD	R12	RHM8.2KGCT-ND	Rohm Semiconductor
0	N/A		R12A, R12B	N/A	
0		RES 1.0K OHM 1/10W 5%			
5	1K	0603 SMD	R13, R51, R52, R106, R108	RHM1.0KGCT-ND	Rohm Semiconductor
		RES 4.7 OHM 1/10W 5%			
4	4.7R	0603 SMD	R14A, R14B, R18A, R18B	RHM4.7GCT-ND	Rohm Semiconductor
		RES 3.9K OHM 1/10W 5%	, , , - , -		
3	3.9K	0603 SMD	R16A, R16B, R107	RHM3.9KGCT-ND	Rohm Semiconductor
			R17A, R17B, R26A, R26B,		
		RES 10K OHM 1/10W 5%	R45, R46, R53, R54, R62,		
13	10K	0603 SMD	R71A, R71B, R104, R105	RHM10KGCT-ND	Rohm Semiconductor
	. –	RES 1.0 OHM 1/8W 5% 0805			
2	1R	SMD	R19A, R19B	RHM1.0ARCT-ND	Rohm Semiconductor
		RES 10 OHM 1W 1% 2512			5 500
2	10R,1W	SMD	R21A, R21B	PT10AECT-ND	Panasonic - ECG
2	33K	RES 33.0K OHM 1/8W 1%	B334 B33B		Dohm Comisonductor
2	JJN	0805 SMD RES 2.2K OHM 1/8W 5%	R22A, R22B	RHM33.0KCRCT-ND	Rohm Semiconductor
2	2.2K	0805 SMD	R24A, R24B	RHM2.2KARCT-ND	Rohm Semiconductor
2	2.21	RES 3.3K OHM 1/10W 5%	N24A, N24D	RI IWIZ.ZRARCI-ND	Romm Semiconductor
2	3.3K	0603 SMD	R27A, R27B	RHM3.3KGCT-ND	Rohm Semiconductor
_		RES 15.0K OHM 1/8W 1%	·····, ····· •		
2	15K	0805 SMD	R30A, R30B	RHM15.0KCRCT-ND	Rohm Semiconductor
		RES 10.0K OHM 1/8W 1%			
5	10K	0805 SMD	R31, R31A, R31B, R40, R41	RHM10.0KCRCT-ND	Rohm Semiconductor
		RES 100 OHM 1W 5% 2512			
4	100R,1W	SMD	R36, R37, R38, R39	PT100XCT-ND	Panasonic - ECG
		RES 470 OHM 1W 5% 2512			
4	470R,1W	SMD	R43, R44, R47, R48	PT470XCT-ND	Panasonic - ECG
_	1-14	RES 47K OHM 1/10W 5%			
5	47K	0603 SMD	R50, R55, R56, R57, R58	RHM47KGCT-ND	Rohm Semiconductor
4	90C	Thermistors - PTC PTC Temp	Baa	504 0204 675 00007	Vishay/BC
1	300	Prot. 90C SWITCH ROTARY SP-3POS	RpA	594-2381-675-20907	Components
1	3way SW	SMICH RUTARY SP-3PUS	S1	401-1962-1-ND	C&K Components
1	SW-PB	6MM LIGHT TOUCH SW H=5	S2	P8010S-ND	Panasonic - ECG
-		POT 200 OHM 3MM CERM		070057500/05	
2	200R VR	SQ TOP SMD	VR1A, VR1B	ST32ETB201CT-ND	Copal Electronics Inc
4	VTAL		N1	400 1100 ND	Murata Electronics
1	XTAL	CER RESONATOR 400KHz	Y1	490-1186-ND	North America
1	XTAL	CER RESONATOR 455KHZ	Y2	490-1187-ND	Murata Electronics
1	ATAL	DIODE ZENER 12V 500MW	12	450-1107-NU	North America
1	12V	SOD-123	Z1	BZT52C12-FDICT-ND	Diodes Inc
I	1 Z V	50D-125	<u>-</u> '	52102012-1 DIGT-IND	


www.irf.com


REFERENCE DESIGN

		DIODE ZENER 51V 410MW			
1	51V	SOD-123	Z3	BZT52C51-FDICT-ND	Diodes Inc
		DIODE ZENER 24V 500MW			
1	24V	SOD-123	Z4	BZT52C24-FDICT-ND	Diodes Inc
		DIODE ZENER 5.6V 500MW		MMSZ5V6T1GOSCT-	
2	5.6V	SOD-123	Z5, Z6	ND	ON Semiconductor

REFERENCE DESIGN

IRAUDAMP10 Hardware

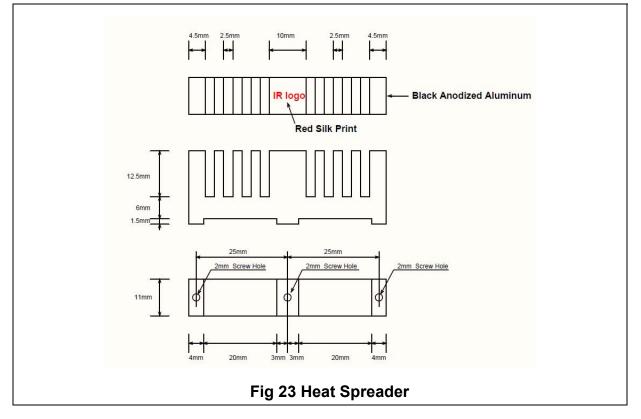

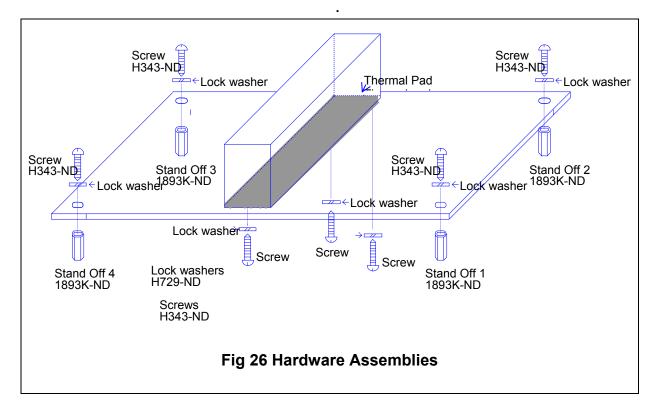

www.irf.com



IRAUDAMP10 PCB Specifications

PCB:

- 1. Two Layers SMT PCB with through holes
- 2. 1/16 thickness
- 3. 2/0 OZ Cu
- 4. FR4 material
- 5. 10 mil lines and spaces
- 6. Solder Mask to be Green enamel EMP110 DBG (CARAPACE) or Enthone Endplate DSR-3241or equivalent.
- 7. Silk Screen to be white epoxy non conductive per IPC-RB 276 Standard.
- 8. All exposed copper must finished with TIN-LEAD Sn 60 or 63 for 100u inches thick.
- 9. Tolerance of PCB size shall be 0.010 –0.000 inches
- 10. Tolerance of all Holes is -.000 + 0.003"
- 11. PCB acceptance criteria as defined for class II PCB'S standards.

Gerber Files Apertures Description:


All Gerber files stored in the attached CD-ROM were generated from Protel Altium Designer Altium Designer 6. Each file name extension means the following:

- 1. .gtl Top copper, top side
- 2. .gbl Bottom copper, bottom side
- 3. .gto Top silk screen
- 4. .gbo Bottom silk screen
- 5. .gts Top Solder Mask
- 6. gbs Bottom Solder Mask
- 7. .gko Keep Out,
- 8. .gm1 Mechanical1
- 9. .gd1 Drill Drawing
- 10. .gg1 Drill locations
- 11. .txt CNC data
- 12. .apr Apertures data

Additional files for assembly that may not be related with Gerber files:


- 13. .pcb PCB file
- 14. bom Bill of materials
- 15. .cpl Components locations
- 16. .sch Schematic
- 17. .csv Pick and Place Components
- 18. .net Net List
- 19. .bak Back up files
- 20. .lib PCB libraries

REFERENCE DESIGN

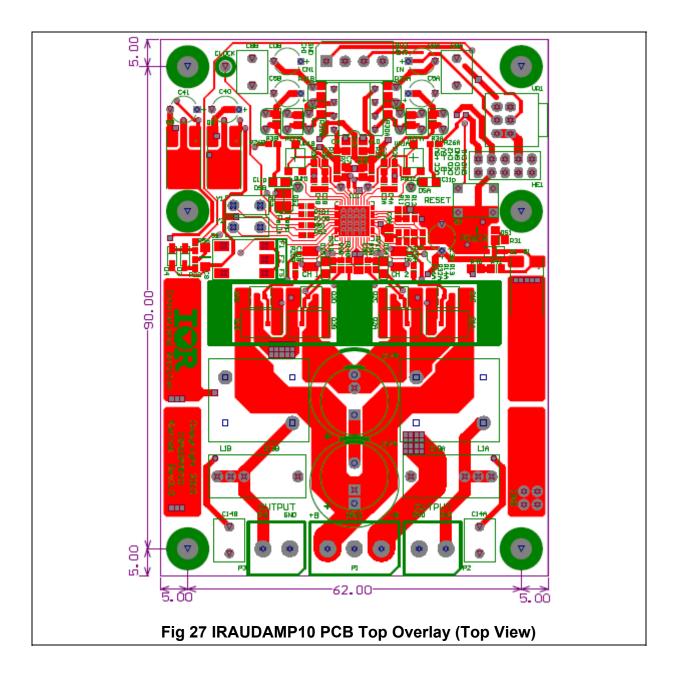

www.irf.com

REFERENCE DESIGN

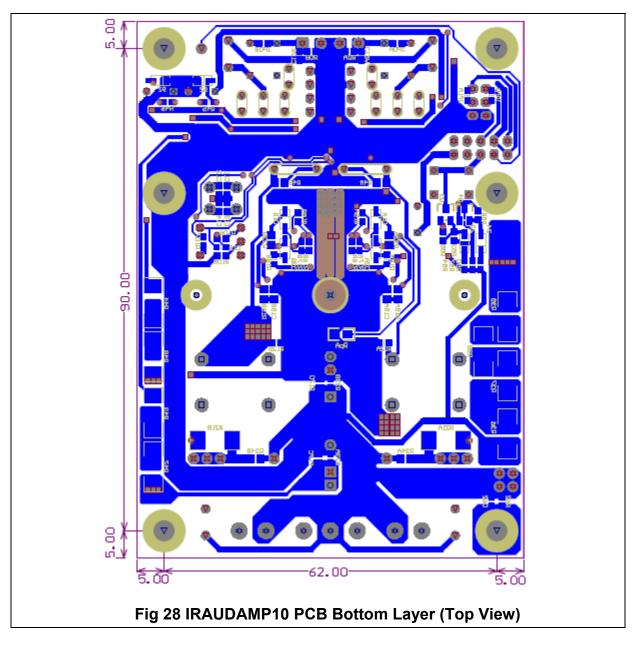

REFERENCE DESIGN

Revision changes descriptions

Revision	Changes description	Date
Rev 1.0	Released	March, 29 2011
Rev 1.1	Correct polarity of XSL pin function in Internal Clock Oscillator	Jan, 25 2012



WORLD HEADQUARTERS: 233 Kansas St., El Segundo, California 90245 Tel: (310) 252-7105 Data and specifications subject to change without notice. 01/29/2009

www.irf.com