

Motorola Semiconductor Application Note

AN1833

A Low-Power Wireless Remote Control Transmitter and Receiver

By C. William Dawson
Semiconductor Products Sector, Woburn, MA
Harry Swanson
Semiconductor Products Sector, Tempe, AZ

Introduction

A low-cost solution for an OOK (on-off keying) transmitter and receiver in the periodic operation part 15 band from 260 to 470 MHz is described in this application note.

The receiver is designed to track and lock to the carrier of a SAW (surface acoustical wave) resonator or crystal-controlled PLL transmitter. The simplest form of ASK (amplitude shift keying) is OOK in which the carrier is simply switched on and off by the PCM (pulse code modulation) waveform. Generally, a low-cost OOK transmitter consists of a SAW resonator and a transistor used as a Colpitts oscillator.

Frequency stability is only fair, compared to a crystal-controlled source, offering excellent frequency stability. Because of poor frequency stability due to time and temperature effects, the frequency of a 300-MHz SAW resonator oscillator typically shifts ± 150 kHz. A standard OOK receiver is designed with a wideband response to capture the drifted transmitter at the expense of sensitivity and selectivity.



The OOK receiver and transmitter presented in this application note offer greater range of operation and more robust data recovery due to improved receiver sensitivity and the receiver's ability to tune automatically to the received carrier from the low-power crystal-controlled transmitter. The transmitter has high-frequency stability and low-harmonics power from unintentional radiators.

NOTE: *Throughout this document, numbers appearing in square brackets ([1], [2], etc.) refer to the information in [References](#).*

Application Overview

In the United States, the Federal Communications Commission (FCC) has allocated the 260- to 470-MHz band for periodic part 15 operation. The FCC regulations are found in the *Code of Federal Regulations* (CFR), title 47, part 15 (paragraph 15.231).

NOTE: *It is strongly recommended that this document be reviewed before pursuing an application in this band.*

In the United States, most of the consumer applications are regulated under part 15, which covers non-licensed intentional radiators. CFR title 47 [1] can be found at most libraries in the reference section or may be obtained from the U.S. Government Printing Office or the Federal Communications Commission's Web site.

Periodic operation refers to the amount of time a system is active. A manually operated transmitter will employ a switch that will deactivate the transmitter automatically within five seconds. Likewise, a transmitter that is activated automatically will cease transmission within five seconds after activation. Periodic transmissions at regular intervals are not allowed. However, polling to determine the integrity of the transmitters used in security or safety applications is allowed if the periodic rate of transmission does not exceed one transmission of more than one second duration per hour for each transmitter in the system.

The field strength of emissions from intentional radiators from 260 to 470 MHz is limited to 12,500 microvolts per meter measured at three

meters. At band edges, the tighter limit of 3750 microvolts per meter applies. Field strength of spurious emissions are 1/10 of the fundamental frequency of the intentional radiator. The bandwidth of the emission shall not be wider than 0.25 percent of the center frequency. Bandwidth is determined at the points 20 dB down from the modulated carrier.

Although continuous transmissions such as voice, video, and data are not permitted, the transmission of recognition codes is allowed. These codes are used to identify a sensor or switch that is activated or to identify the particular component as being part of the system. The intentional radiator is restricted to the transmission of control signals such as those used with security alarm systems, door openers, keyless entry, remote switches, and remote sensing/telemetry, etc.

The general system may consist of a number of transmitters used to provide control signals from remote sites. The receiver demodulates the signal and recognizes the remote sites; then the system may initiate a response in several ways such as sounding an alarm, making an automatic distress call, turning on a light, opening a door, and turning on sprinklers, etc. Each site may use a coded address that would be broadcast to indicate the intended receiver. Some applications are more critical than others, such as a security alarm or distress calling systems. It is essential that the system is dependable.

The receiver has the job of extracting and reproducing information from the modulated RF (radio frequency) signal that has been corrupted by noise in the channel. Consistent recovery and error-free replication of the modulating signal requires a receiver which has reliable performance.

The two main classes of radio frequency receivers are:

- Tuned radio frequency (TRF)
- Superheterodyne receivers

The TRF receiver may consist of several cascaded high gain RF amplifier and tunable bandpass filter stages followed by an appropriate detector (envelope detector, product detector, FM (frequency modulation) detector, etc.). A reliable TRF receiver at UHF (ultra-high frequency) frequencies is difficult to achieve because appreciable

parasitic feedback between the output and input of the high gain RF amplifier chain creates oscillation at the center frequency. Reducing the gain in the RF amplifier chain may prevent oscillations but lower gain will reduce the sensitivity of the receiver. These receivers generally use discrete semiconductors since integrated circuits are not available for low-voltage, low-power applications.

The more reliable and stable receiver described in this application note is a superheterodyne type receiver. In this receiver, the RF carrier is filtered and amplified using an RF preamplifier and is down converted using a mixer and local oscillator (LO) to a convenient, lower frequency called the intermediate frequency (IF). The IF signal is amplified and filtered and then demodulated by using an appropriate detector.

The OOK receiver shown in **Figure 1a** has many advantages over a TRF receiver. It utilizes two monolithic integrated circuits (IC), the MC13144 [2] as a cascade low-noise amplifier (LNA), and the MC13158 [3] as the main building block components of the receiver. This receiver offers very stable operation with more than 115 dB of stable gain. Typical sensitivity is -100 dBm which allows for a greater operating distance between transmitter and receiver. By utilizing a varactor-controlled LO locked by an external automatic frequency control (AFC) circuit, the receiver has the ability to lock onto the transmitter. Thus, this receiver system has no need to use a more expensive crystal oscillator for the LO.

The OOK transmitter (**Figure 1b**) is implemented by using a versatile 1-chip, fixed frequency PLL (phase-locked loop) system IC, the MC13176D [4] which operates under an inexpensive crystal reference source from a microcontroller unit, the MC68HC705J1A [5].

Baseband processing functions are performed by MCUs in both the remote receiver and handheld transmitter.

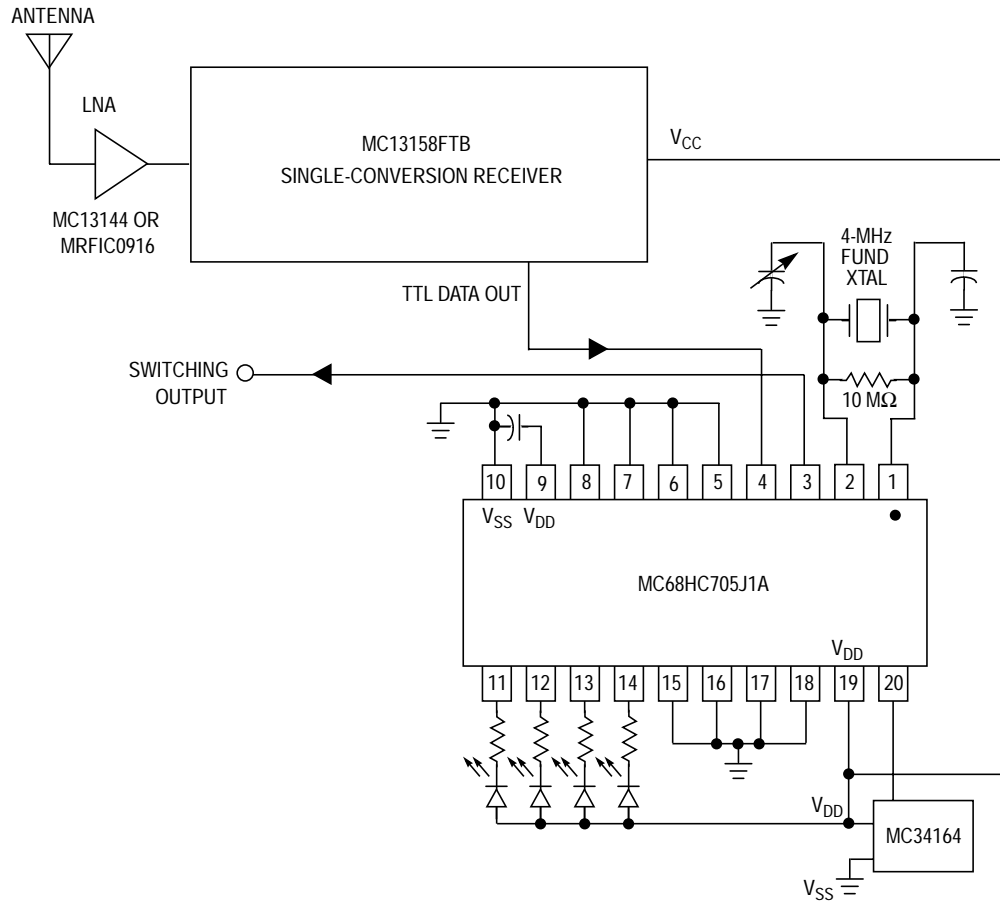


Figure 1a. OOK Receiver Block Diagram

Freescale Semiconductor, Inc.

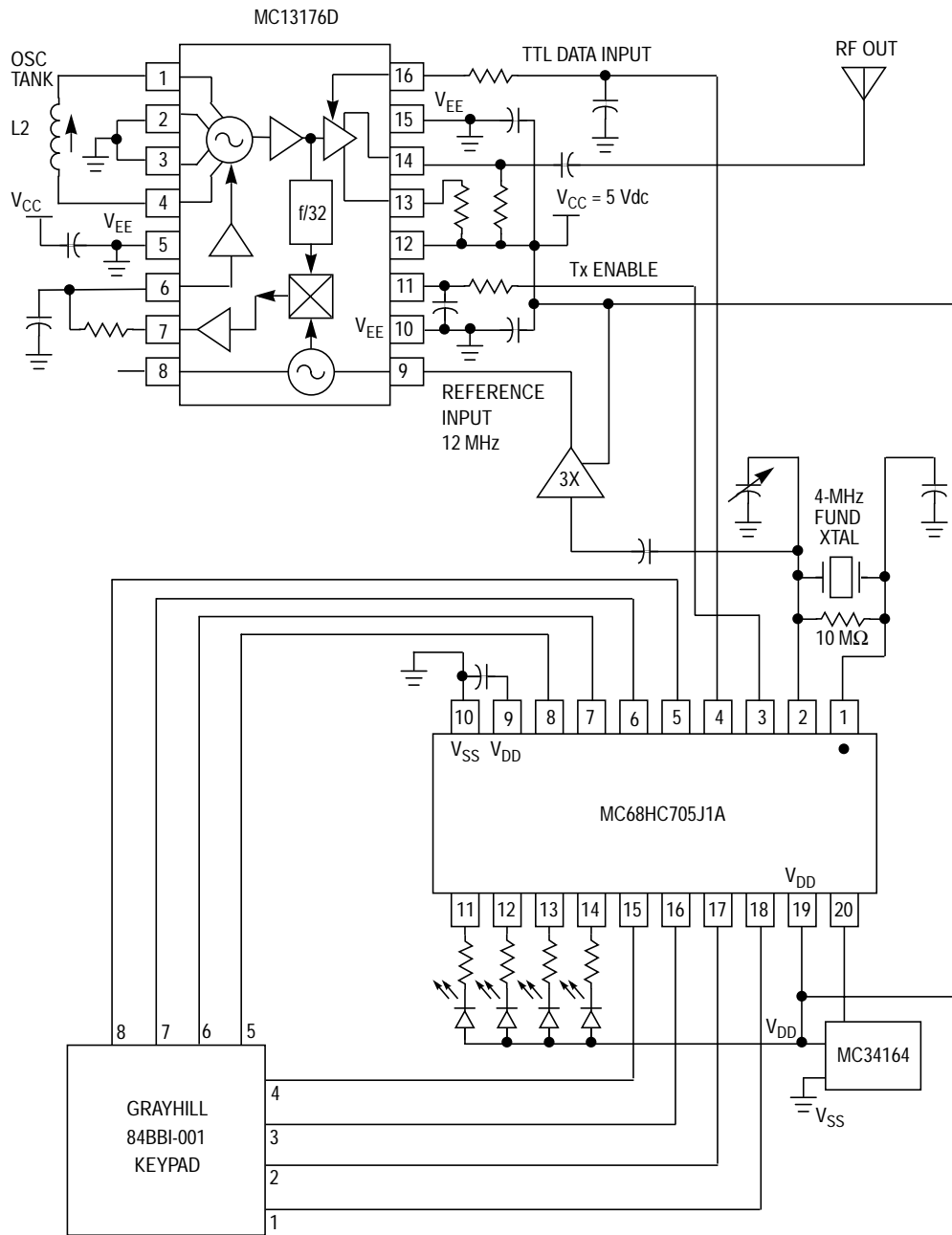


Figure 1b. OOK Transmitter Block Diagram

Freescale Semiconductor, Inc.

Description of the MC13158

The MC13158 is an integrated, single-conversion, wideband FM receiver system intended for digital and analog modulation formats. It was developed as a high-performance IC to be used in battery-operated radio systems, as it can be operated below 2 Vdc. The MC13158 is available in a 32-lead, low-profile quad flat package (LQFP), which offers small size layout and stable performance.

While it is an ideal receiver for the recovery of GFSK (Gaussian-filtered shift keying), FSK (frequency-shift keying), or FM (frequency modulation) signals, the circuit detailed in this application note shows how the MC13158 system can be reconfigured to recover OOK signals. Further details about the MC13158 not covered in this application note are found in comprehensive device documentation [2].

The MC13158 functional blocks include:

- Differential input mixer
- 40-dB IF amplifier
- 55-dB limiter amplifier
- Externally tuned FM quadrature detector
- Received signal strength indicator (RSSI)
- Data slicer comparator
- Carrier detection

The mixer has differential RF inputs allowing it to be used in balanced and single-ended configurations. Its single-ended input impedance is 1 k Ω in parallel with 4 picoFarads. Access is provided to the base and emitter of the MC13158 internal oscillator transistor for attaching the oscillator resonant tank circuit. The oscillator transistor internally drives the mixer and can be operated as an LC oscillator to greater than 450 MHz. The application circuit (see [Figure 2](#)) uses a varactor-controlled oscillator (VCO) to provide LO drive at approximately 395 MHz.

The IF chain is split into two sections to allow IF bandpass filtering in two places:

1. Between the mixer and IF amplifier
2. Between the IF and limiter amplifiers

Output impedance driving each filter port is $330\ \Omega$, which is ideal for common ceramic IF filters centered at 10.7 MHz. The IF and limiter amplifier's internal inputs are $330\ \Omega$ to ground to match the 10.7-MHz ceramic filters.

The limiter is coupled internally to the quadrature detector inputs, and it is also pinned out. An external RLC (resistance-inductance-capacitance) tank provides selection of the demodulator tuned frequency and detection bandwidth. The detected signal is brought out by the inverting amplifier buffer. Its output amplitude swing is set by an external feedback resistor from the output (pin 17) to the input of the inverting amplifier (pin 15). It is combined with a second resistor from the input to the negative supply (pin 16) to select the output dc level.

The RSSI (received signal strength indicator) output provides an output current that is proportionate to the logarithm of the receiver input voltage.

NOTE: *Externally load it with a resistor to V_{EE} .*

Its typical transfer gain is $0.4\ \mu\text{A}$ per dB of input drive level. The RSSI dynamic range is higher than 70 dB, which is achieved by sensing signal strength at each stage of the IF and limiter amplifiers and summing them together. The RSSI linearity is affected by the loss placed between the IF amplifier and the limiter amplifier; a total midband attenuation of 10 dB is optimal.

The data slicer comparator has more than 500 kHz of toggling capability. Its inverting input (pin 18) and non-inverting input (pin 20) have back-to-back diodes across them. The recovered signal may be dc coupled to one data slicer input while the other one is ac grounded; it is allowed to swing $\pm 1\ V_{BE}$ about the dc level to the comparator input.

The polarity of the output data depends on which input is referenced to V_{EE} (ground). For positive logic data output, the data signal goes to the non-inverting input. Where the reference input pin of the data slicer is


capacitively grounded, the size of this capacitor and the nature of the data signal determine how faithfully the data slicer shapes up the recovered signal. A control pin is provided to shut the data slicer output off (DS off, pin 19).

Receiver Application Circuit Description/Design

The block diagram of the OOK receiver and its controller is shown in **Figure 1a**. The complete schematic of the MC13144 and MC13158 single conversion OOK receiver circuit is shown in **Figure 2**. The internal on-board transistor is used as the LO source to down convert the received 384-MHz RF carrier signal. Its VCO tuning frequency is controlled by an automatic frequency control (AFC) circuit created with the dc output from the MC13158 quadrature detector buffer amplifier and an external loop filter.

OOK demodulation is achieved by using the MC13158 fast RSSI port. The RSSI output is fed to the data slicer, which shapes the recovered RSSI data into a rail-to-rail logic swing.

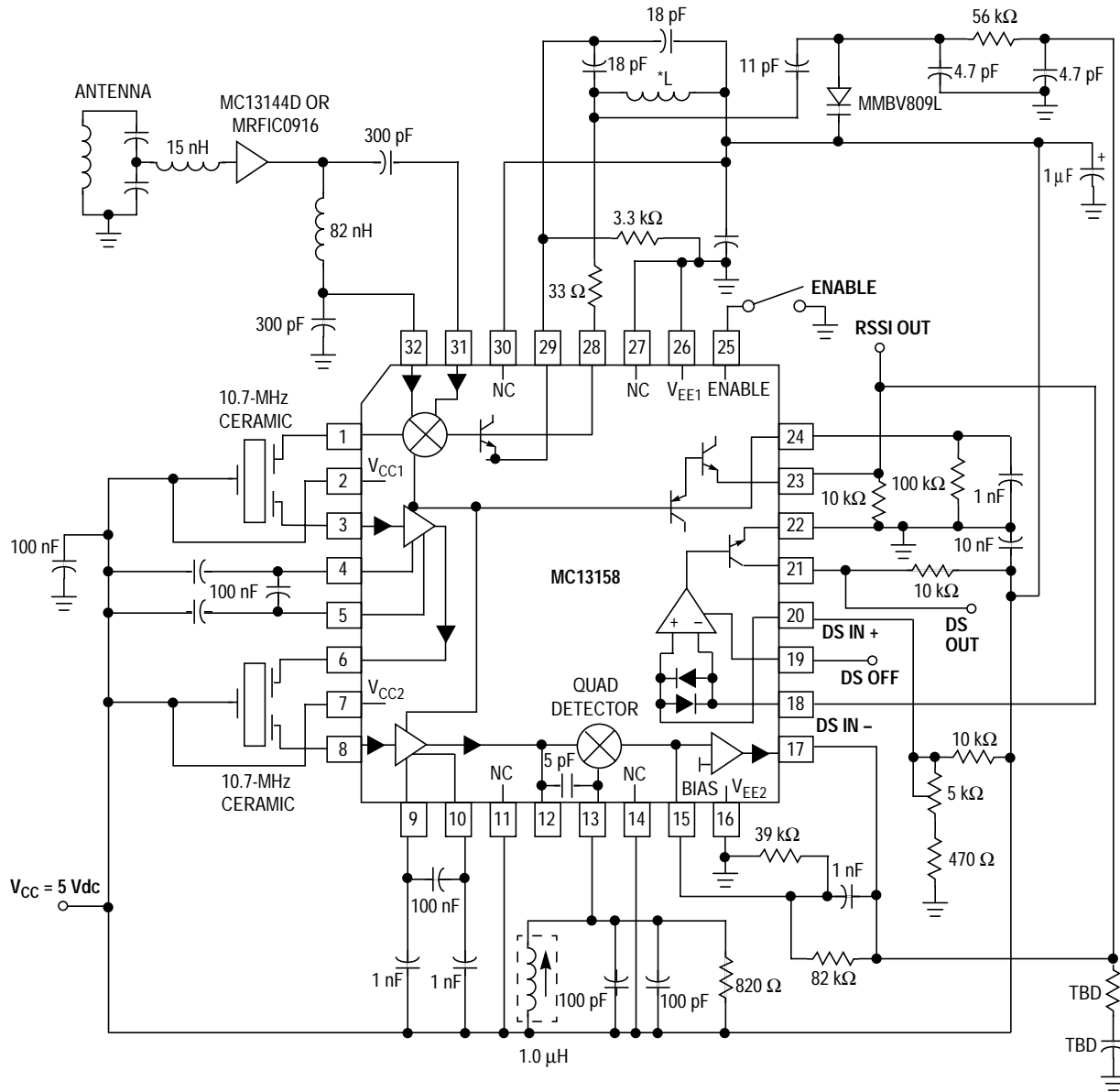In the following sections, each part of the OOK receiver is explained in more detail.



* L is 5T #28AWG enameled wire wound on a #74 drill bit.

Figure 2. Detailed OOK Receiver Circuit

External Varactor Controlled Local Oscillator

Figure 3 is a schematic of the receiver external local oscillator circuit. For easy reference, the components are labelled in the following discussion.

The LC oscillator uses the on-board transistor. The MMBV809L is a low-voltage varactor suitable for UHF applications; it is a single varactor in an SOT-23 package. This oscillator is tunable over a range of approximately 1.5 MHz (393.8 to 395.3 MHz) with the control voltage V_{VCO} from the AFC.

Figure 4 is a curve of VCO frequency versus AFC V_{VCO} . Note that the VCO frequency decreases with increasing control voltage since the varactor diode cathode is taken to V_{CC} and the control voltage is applied to the anode.

This circuit is breadboarded using a custom PC board in which the RF ground is V_{CC} and RF path lengths are minimized. High quality surface mount components were used except where otherwise specified. The absolute values of the components used will vary with layout placement and component parasitics.

In the VCO circuit, R1 is the emitter bias resistor. R2 forms the base bias circuit. C1 and C2 make up the Colpitts capacitive divider network. CS and CB are capacitive trimmers for the LC oscillator. The shunt capacitor CS across the varactor diode, MMBV809L [6], and series capacitor CB are used to adjust the tuning range by varying the capacitance of the LC oscillator circuit.

This equation shows the relationship:

$$1. \quad f = (0.159) / [\{ [[(C1)(C2)] / [(C1 + C2)] + C] * [L] \}^{1/2}]$$

where C is the equivalent capacitance of CB, CS, and CV.

The relationship for C is:

$$2. \quad C = (CS + CV)(CB) / (CB + CS + CV)$$

The oscillator tuning range is controlled by ΔC resulting from the voltage variable ΔCV . The following equation by similarity to equation (2) above shows this relationship.

$$3. \quad \Delta C = (CS + \Delta CV)(CB) / (CB + CS + \Delta CV)$$

The oscillator operating frequency may be estimated by the next equation, which is derived by substituting equation (2) for C in equation (1).

$$4. \quad f = (0.159) / [\{ [[(C1)(C2)] / [(C1 + C2)] + [(CS + CV)(CB) / (CB + CS + CV)] * [L] \}^{1/2}$$

Solving (4) for L, results in:

$$5. \quad L = (0.159)^2 / \{ [[(C1)(C2)] / [(C1 + C2)] + [(CS + CV)(CB) / (CB + CS + CV)] * f^2 \}$$

where $C1 = C2 = 18 \text{ pF}$


$$CS = 4.7 \text{ pF}$$

$$CV = 5 \text{ pF (at 2.2 Vdc)}$$

$$CB = 11 \text{ pF}$$

For an oscillator center frequency of 394.7 MHz (high side LO is used), the value of L is calculated to be 11.5 nH.

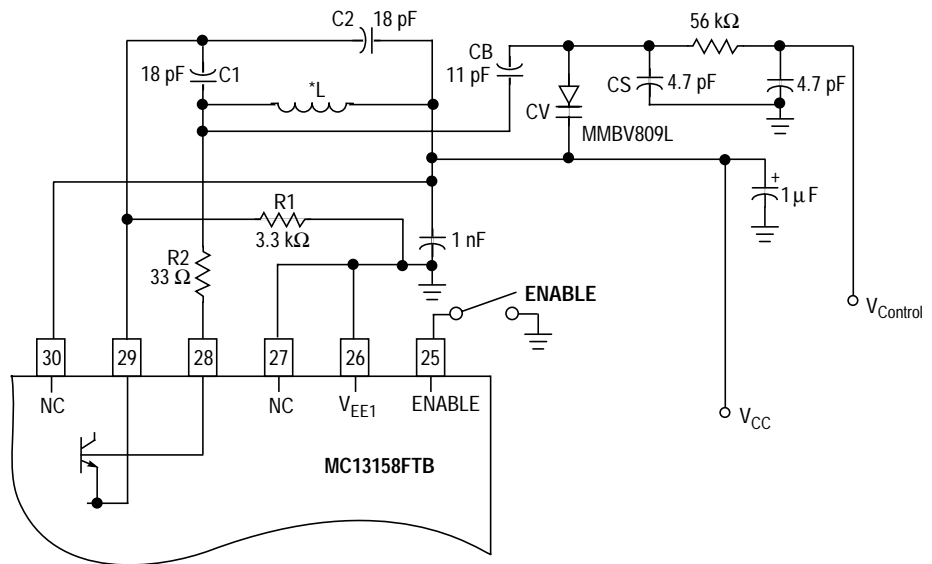For a more in-depth study, Randall Rhea discusses several oscillator circuits in his book on oscillator design [7].



* L is 5T #28AWG enameled wire wound on a #74 drill bit. The VCO is fine tuned by adjusting the spacing between windings of this air core inductor.

Figure 3. Receiver 394.7-MHz Local Oscillator

 


Figure 4. VCO Frequency versus VCO Control Voltage

Automatic Frequency Control

The MC13158 OOK receiver uses automatic frequency control (AFC) to adjust the VCO with respect to the RF to down convert it to the desired IF frequency. The VCO's output frequency is adjusted by the output voltage from a quadrature detector buffer amplifier circuit and the loop filter. The loop filter input is taken from the buffered output of the frequency discriminator of the MC13158. The discriminator V_{Out} versus frequency response is set by the resonant frequency and bandwidth of the external quadrature tank circuit; while the dc output component is determined by the combination of the external load feedback resistor, R17, and the resistor from inverting input to ground, R15.

The detector dc level, V17, is calculated in this equation:

$$V17 = \{ [(R15/R17) + 1] / (R15/R17) \} * V_{BE}$$

where V_{BE} is a diode drop = 0.75 Vdc.

In the application circuit, a V17 of nominally 2.2 Vdc is chosen, yielding standard resistor values for R17 of 82 k Ω and R15 of 39 k Ω .

The AFC loop gain and settling time are set by the buffer amplifier feedback resistor and the capacitor, respectively. The values of these loop characteristics are left to the designer's discretion, depending on the system requirements. Stable frequency acquisition responses within milliseconds have been achieved with the schematic values of this simple single-pole circuit.

The closed loop frequency error is 12 kHz per 100 kHz change in RF frequency. This provides:

- A bias to the discriminator output
- An offset to dc match the loop filter frequency versus voltage out response to VCO control characteristic

The AFC output (varactor control voltage) decreases with increasing IF frequency. This system was designed for high side mixer conversion (the LO is above the RF). The ground reference of the varactor is taken

to V_{CC} (ac ground); thus, the LO frequency increases as the varactor control voltage decreases.

The RLC values shown will tune the tank to 10.7 MHz and allow for approximately 900-kHz AFC tuning bandwidth. **Figure 8** shows the pull-in and hold-in range of the AFC loop. An adjustable coil is used to tune the quadrature detector. The resistor sets the bandwidth by lowering the Q of the LCR tank circuit. The following relationship shows how to calculate the response of the discriminator resonant tank.

$$6. \quad Q = R / X_L$$

$$\text{for } R = 820 \, \Omega; X_L = 2\pi(10.7)(1.0) = 67.2 \, \Omega$$

$$\text{then } Q \sim 12.2$$

$$7. \quad \text{BW } 3 \text{ dB} = f_o / Q$$

$$\text{thus, the 3-dB bandwidth} = 10.7 \text{ MHz} / 12.2 = 880 \text{ kHz}$$

Should the overall transmit/receive system be prone to extreme frequency drift, the quadrature coil circuit bandwidth may need to be increased to provide adequate tracking range.

IF Interstage Filtering

Ceramic bandpass filters are placed between:

- Mixer output and the IF amplifier input
- IF output and the limiter input (see **Figure 2**)

They allow improved sensitivity by bandwidth, limiting the noise to the RSSI detectors, especially the limiter. The filters shown in the schematic have a 3-dB bandpass response centered at 10.7 MHz which is 280 kHz wide. Choice of IF filter bandwidth will affect the fidelity of the recovered baseband signals. As the data rate is increased, the filter bandwidth should be wider.

The filter bandwidth is affected by its source impedance and output load impedances which are 330 Ω . The MC13158 mixer output and IF amplifier input and output impedances are 330 Ω to match typical 10.7-MHz ceramic filters.

Data Recovery Circuit

The received OOK signal is converted from RF to baseband by the MC13158 RSSI function. The RSSI output sources a current to an external load connected to V_{EE} to produce a voltage. The choice of this load resistance affects the receiver performance. Obviously, the resulting RSSI gain (V_{Out}/RF_{In}) is directly proportionate to this load. When this load is large enough, the RSSI output will saturate, which will compress the high RF input end of the RSSI transfer response. A load of 100 k Ω is a good choice to obtain 70 dB of monotonic RSSI dynamic range with no compression. The load impedance chosen also affects the RSSI rise and fall times (see [Figure 5](#)). The RSSI output rise and fall times are more than adequate to follow signal amplitude variations to rates greater than 50 kHz.

For data rates of 10 kHz or less, 680 pF and 100 k may be connected from pin 24 to V_{EE} . These components form a low pass filter with its corner at approximately 10 kHz; this helps clean up the RSSI response under low signal conditions. Data rates up to 50 kHz have been achieved without low pass filtering.

The RSSI is dc coupled to the data slicer non-inverting input (pin 20). The data slicer inverting input terminal is referenced to V_{EE} with a voltage divider or a diode to ground. Temperature stability of this reference should be considered for receiver operating over an extended temperature range.

The data slicer can be disabled by connecting the data slicer off pin to greater than 1.5 Vdc (V_{CC} will suffice). Should the receiver system be integrated with a transmitter, this will prevent an invalid data slicer output from causing problems.

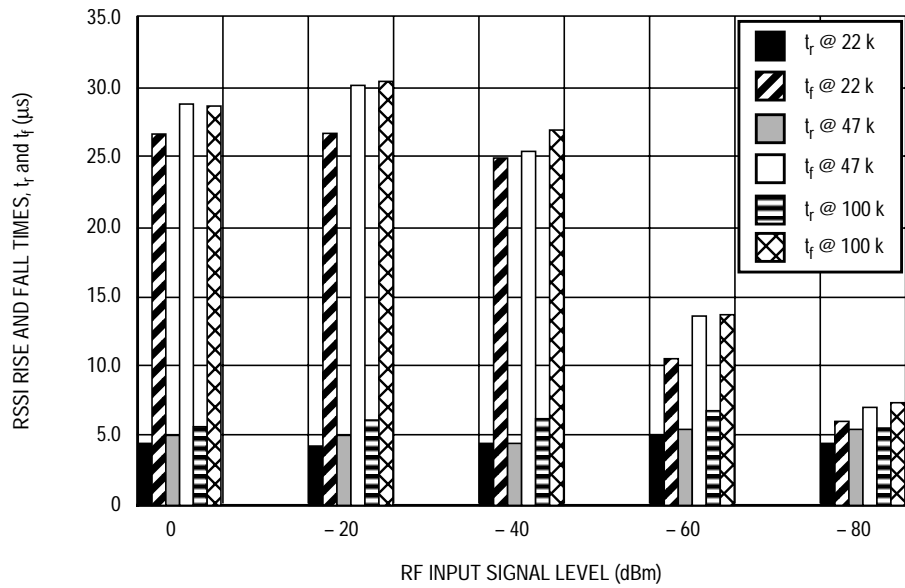


Figure 5. RSSI Output Rise and Fall Times versus RF Input Signal Level

Low-Power Transmitter

The schematic in **Figure 6** shows the handheld OOK transmitter circuit. It is comprised of the MC13176 UHF PLL transmitter, the MC68HC705J1A MCU, and the reference/tripler.

The PLL reference at pin 9 is derived from tripling the 4-MHz crystal reference from the MCU. In this tripler, a low-cost transistor, MMBT3904L [8], is used with a 7-mm shielded transformer that provides the 12-MHz resonant LC tank at the output of the transistor and also the means to easily supply dc to the collector output. The transformer is a part supplied by Toko America [9] (part number 600GCS-8519N). Twelve MHz, the third harmonic from the 4-MHz crystal, is selected by the LC resonant circuit formed by the primary windings between pins 1 and 2 of the transformer and an external capacitor of 330 pF.

The secondary output of the transformer uses a tapped capacitor transformer to provide a lower source impedance to the reference input of the MC13176 (pin 9) while forming a second LC resonant network. Thus, the tripler circuit is a double tuned LC network which provides increased selectivity of the 12-MHz signal.

The MC13176 is enabled by the MCU at pin 10 and data is input at pin 16 creating the OOK modulation. At pins 1 and 4, an external inductor is used as the resonator for the current controlled oscillator (CCO). This RF resonator must be a high Q component and adjustable to align the CCO to the reference source.

The application circuit uses a Coilcraft adjustable 7-mm shielded inductor [10] (part number 150-04J08S).

Phase noise of the MC13176 measures at -85 dBc/Hz at 10-kHz separation (**Figure 7**). This offers ample performance for a wideband system such as described in this application note.

Layout and Practical Considerations

These layout considerations are suggested:

1. Use double sided PCB in which one side is the circuit side where all surface mounted components are placed and where the interconnect and circuit traces are done; the other side is the V_{EE} ground side where leaded components are mounted and only a few necessary circuit traces are done.
2. Keep all RF traces as short as possible.
3. Avoid point-to-point wiring; it is best to run the trace on the PCB.
4. Use controlled impedance microstrip lines in high frequency portions of the circuit.
5. Use ground return paths through ample size holes to the ground side of the PCB.
6. Decouple V_{EE} where the pins of the IC contact the trace on the PCB.

In mixed signal applications, isolation of the digital and RF ground and supply lines is a must. In addition, the receiver is properly shielded and ac decoupled to eliminate interference by switching and high EMI/RFI sources.

Performance in Application Circuit

In the receiver, an input carrier level of -80 dBm allows recovery of the PCM waveform without jitter or tearing at 2 kbps (see **Figure 2**). This is improved approximately 15 dB by using a preamp and bandpass filtering before the mixer. Design of the matching network to the preamplifier should consider interfacing to an antenna which would be "application specific," depending on the size and type of antenna. A loop antenna suitable for this application is discussed in a book by Constantine Balanis [11].

The pull-in range and hold-in range are dependent on the input drive level. In general, under higher drive the hold-in and pull-in ranges are greater. **Figure 8** shows a plot of the hold-in range and pull-in range versus the RF input level. The pull-in range is consistent with the selectivity of the IF bandwidth.

The application circuit supports data rates up to 50 kHz. This has been confirmed in the lab with relaxed interstage and baseband filtering. The wider filtering is much more susceptible to interference.

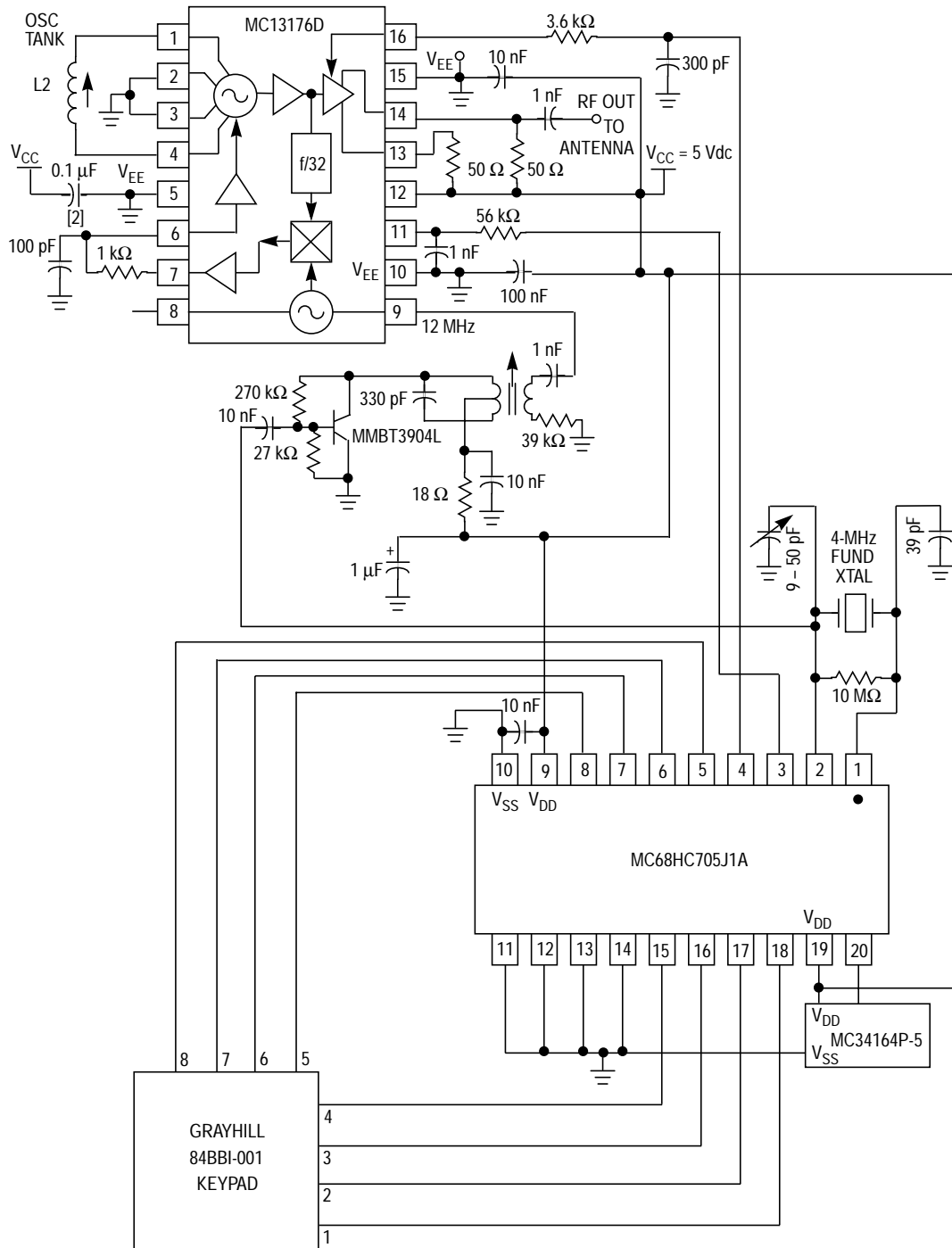


Figure 6. 384-MHz OOK Transmitter

 


Figure 7. Phase Noise versus Frequency

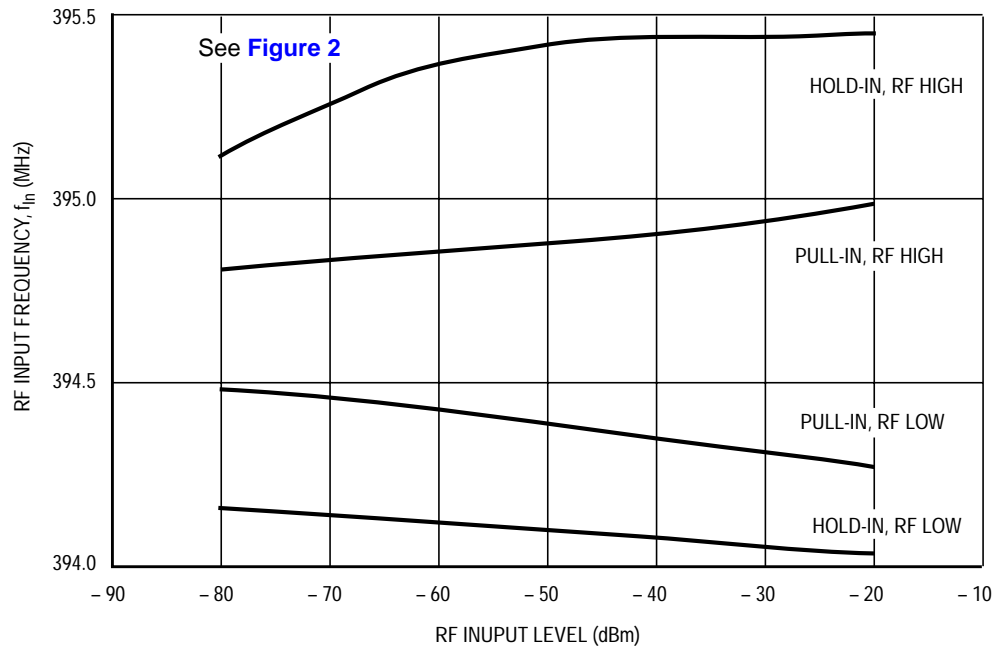


Figure 8. AFC Capability: Hold-In and Pull-In Limits versus RF Input Level

MCU Introduction

A low-power wireless remote control system has four pieces:

1. Method of initiating a request such as a button on a remote control unit
2. Sending a message from an RF transmitter
3. Receiving and validating a message
4. Determining action to be taken such as releasing a solenoid or turning on a light

The microcontroller unit (MCU) in the remote control unit decodes the button that has been pressed and sends a bitstream to an RF transmitter. The receiver acquires the RF bitstream, converts it to digital format for an MCU, which analyzes the digital data, and determines what operation is to be performed.

Microcontroller Software Overview: Initiate an Access Request

A battery-powered remote control unit waits in an extremely low-power or sleep mode until someone presses a button or series of buttons on the unit. (Low-power mode means a battery will power the unit longer.) Pressing buttons causes the MCU to wake up and begin executing an internal sequence of commands that determine what keys have been pressed. The MCU in this design is an MC68HC705J1A [5]. The keystrokes are stored by the MCU and determine the format of an access request message.

Interrupt Service Routine

When a keypad button is pressed, it asserts an input pin that triggers the execution of the interrupt service routine (ISR). The MCU clock feeding the MC13176 turns on when a keypad button is depressed. Decoding of which key is depressed is done using the routines written by David Yoder [12]. The ISR examines the port A input values when certain port B outputs are asserted.

Sending a Message

When two keypad values have been received, the MCU ensures a logic low is on the TTL (transistor-to-transistor logic) data input to the transmitter and enables the MC13176 via output pins on port B. After waiting for the transmitter to warm up, a logic 1 is presented to the TTL data inputs of the MC13176 for a 500-microsecond interval representing a “front porch.” Three preamble characters (55 hex) and the two keypad values received are sent serially to the transmitter by the MC68HC705J1A using the routines written by Scott George [13]. The MCU turns off the transmitter enable pin on port B, initializes all software flags and buffers, prepares for the next keypad interrupt, and then re-enters sleep mode. The transmitter flowchart is shown in [Figure 9](#) and [Figure 10](#).

Acquire and Validate an Access Request

The receiver activates itself when it sees a specific signal exceed a strength threshold and passes the data bits received in a digital format to an MCU input port. When the MCU sees at least a 500-microsecond logic 1 on the receiver input pin, a “shutter timer” is activated that has a timing interval equal to 8.2 milliseconds.

The MC68HC705J1A examines the received data, using the routines written by Scott George [13], for ASCII character sequences of:

- Start bit
- Eight bits of logic high or low data, and
- A stop bit during the “shutter timer” period

The character data is put together via several subroutines and placed in the MCU buffer memory. Data acquisition is terminated when an interrupt caused by the “shutter timer” interval expiring occurs. The receiver flowchart is shown in [Figure 11](#), [Figure 12](#), and [Figure 13](#).

Permit or Reject Access

The receiver buffer is examined for a specific data sequence when data acquisition is terminated. If at least two of the preamble characters are received as alternating data bits of logic 1 and 0 (ASCII 55 hex) and the receiver number or a broadcast number is in the lower nibble of the address byte, then the MCU will perform actions specified in the command byte.

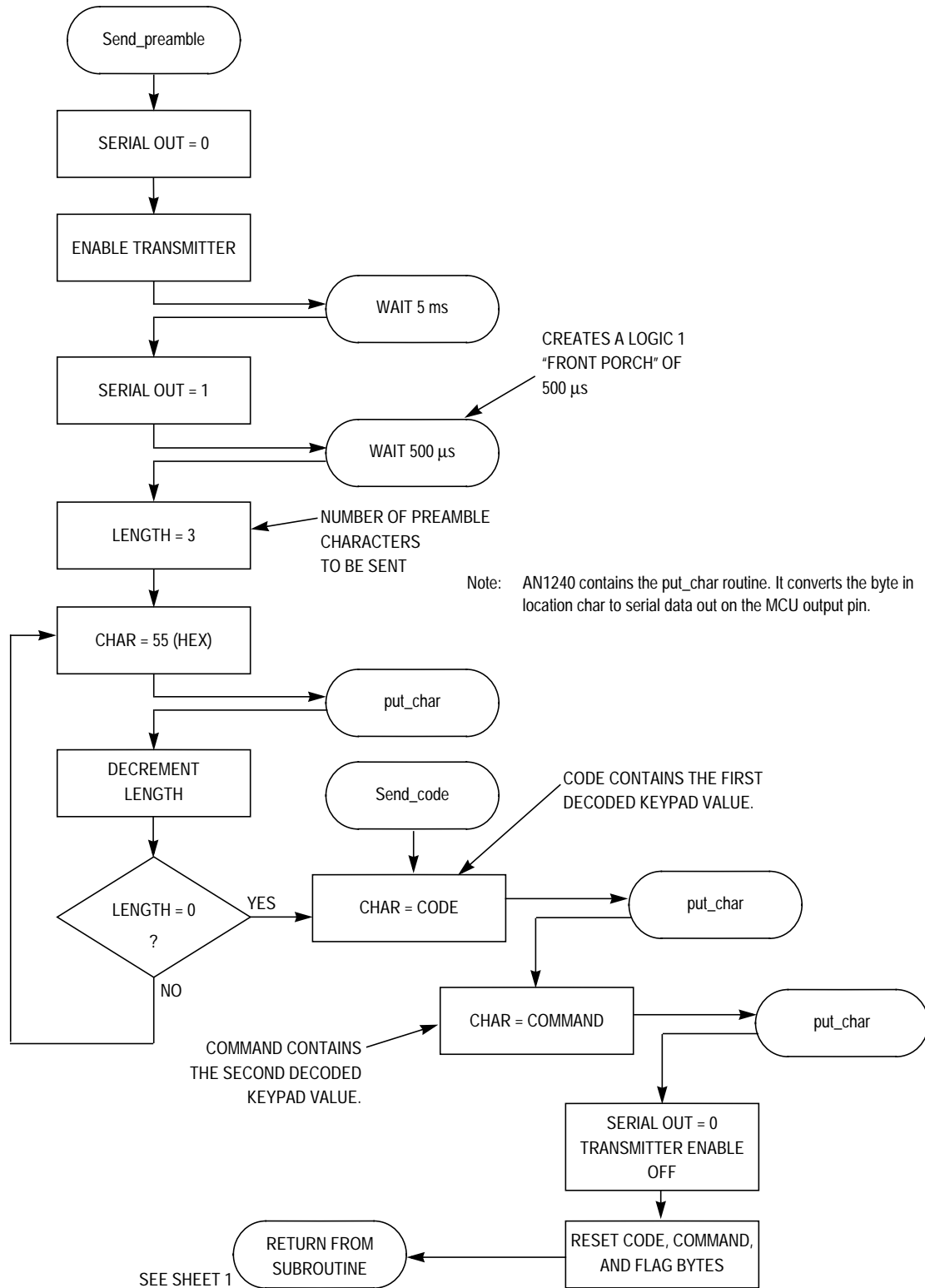


Figure 10. Transmitter MCU Flowchart (Sheet 2 of 2)

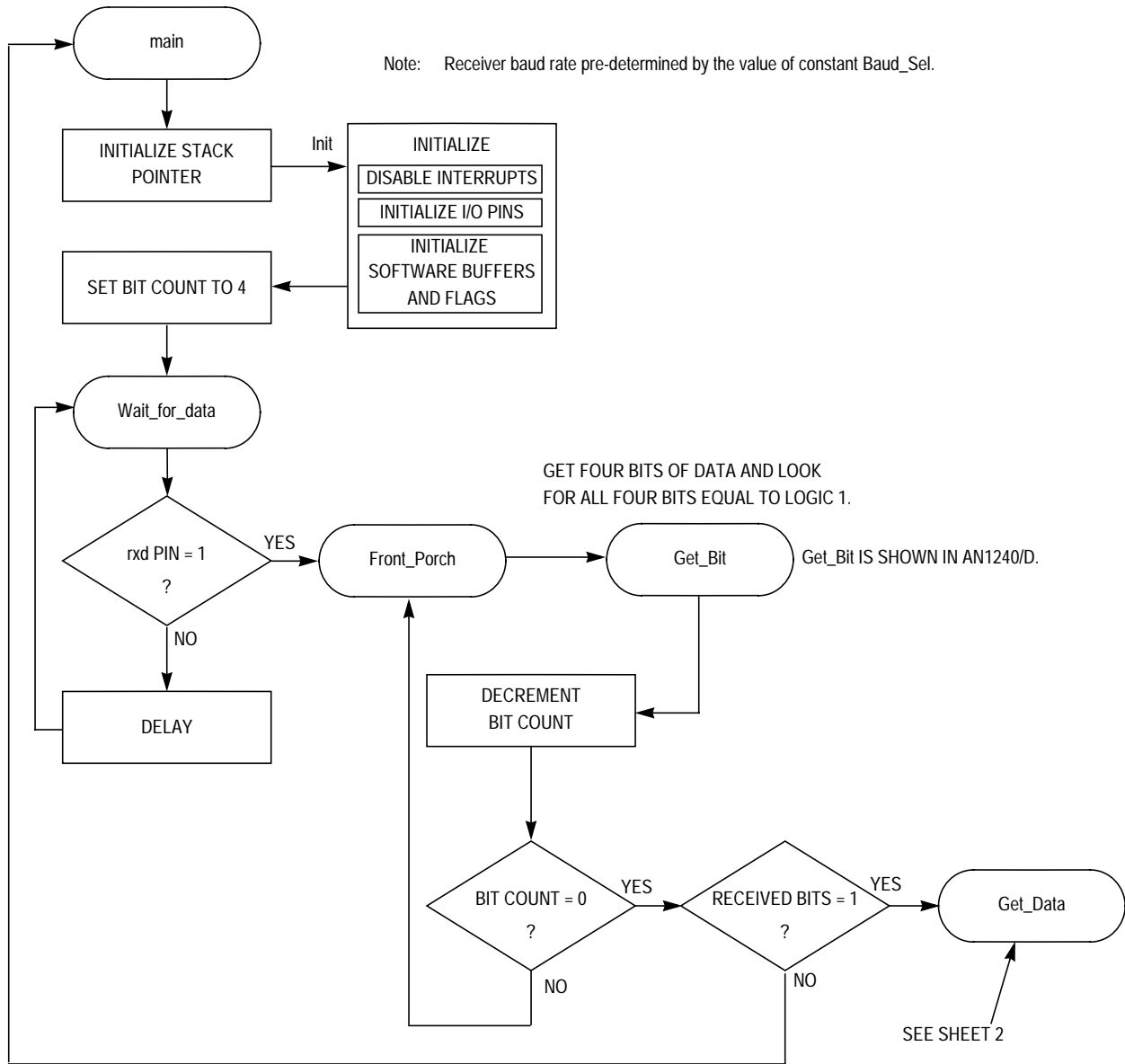


Figure 11. Receiver MCU Flowchart (Sheet 1 of 3)

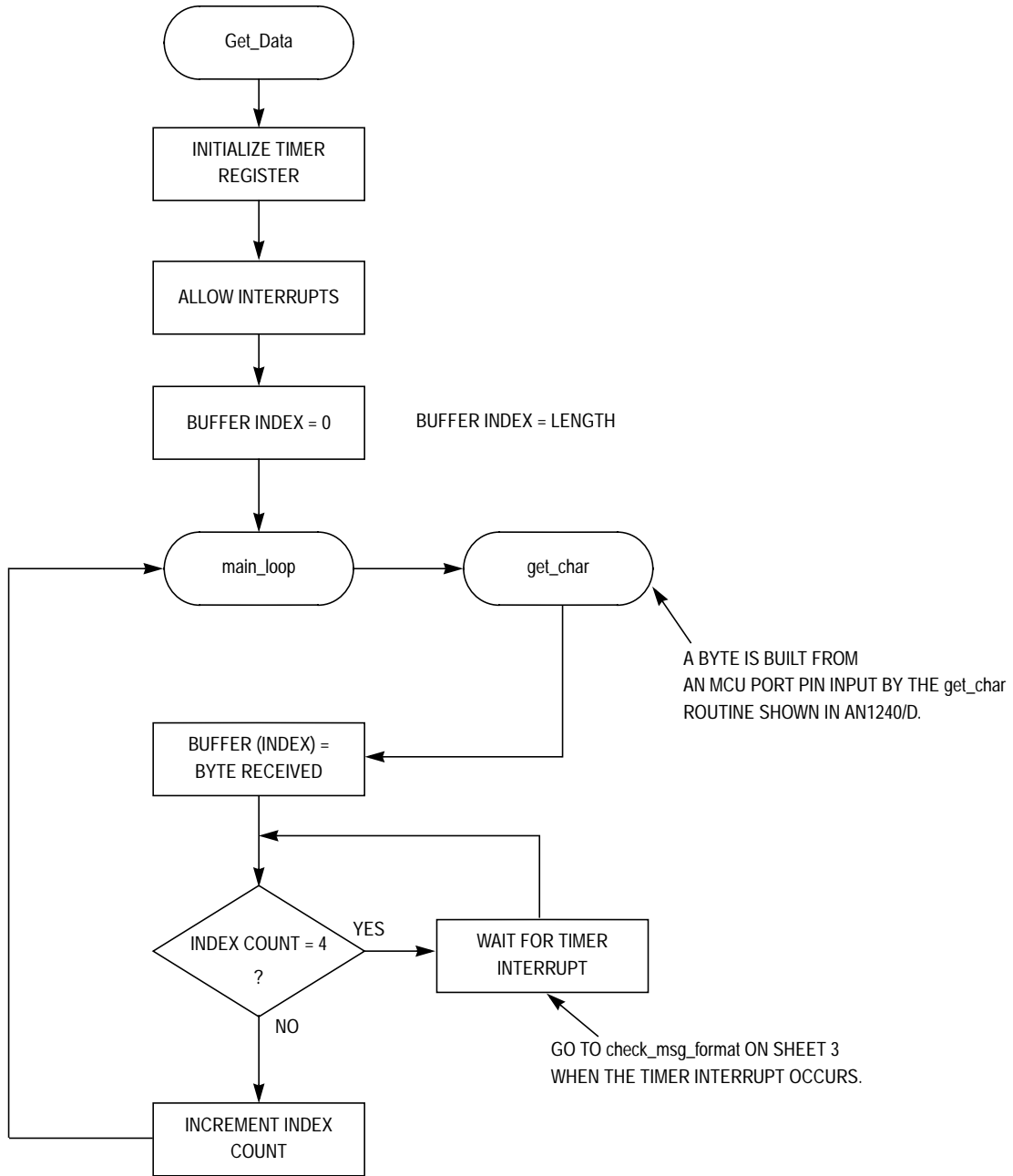


Figure 12. Receiver MCU Flowchart (Sheet 2 of 3)

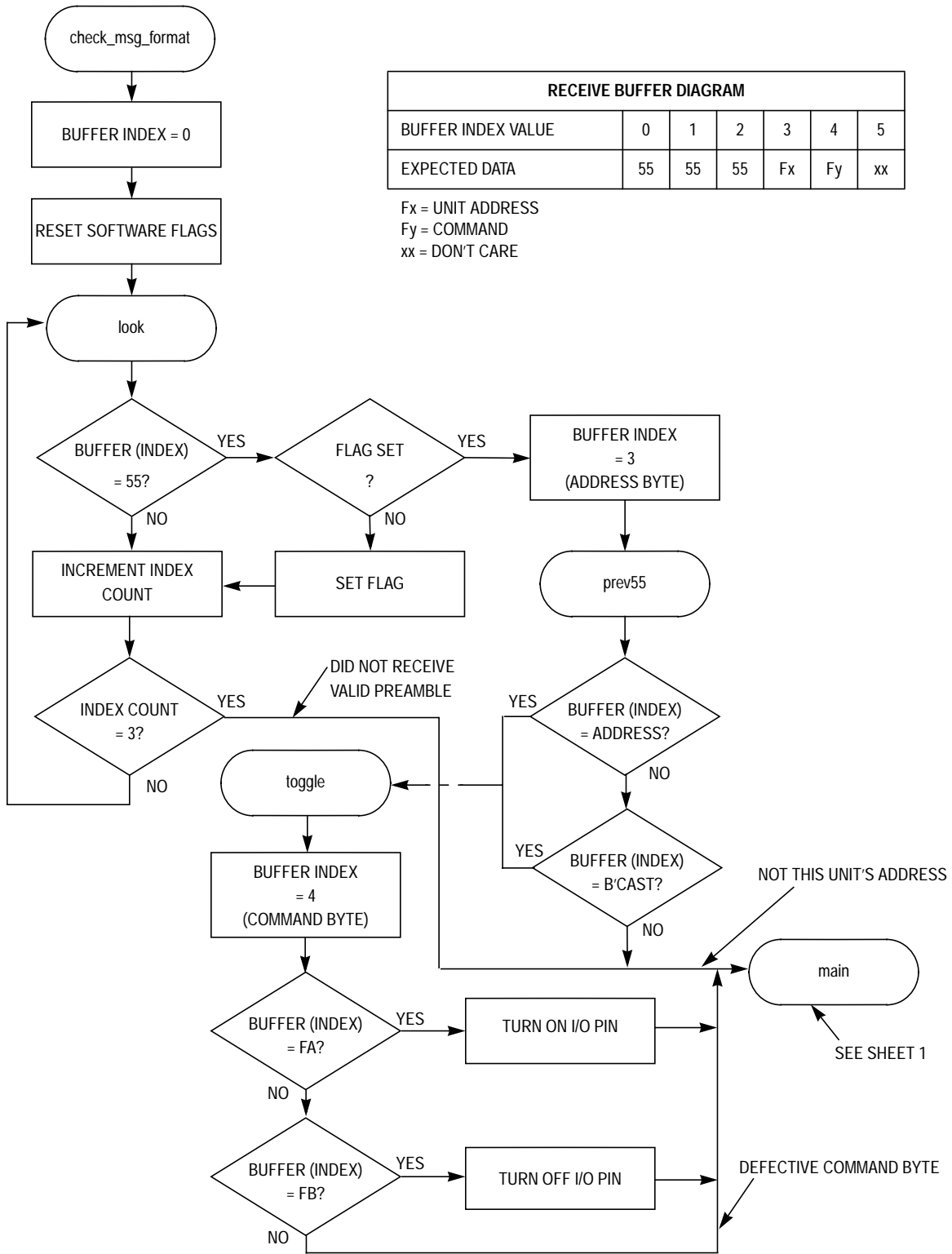


Figure 13. Receiver MCU Flowchart (Sheet 3 of 3)

Conclusions

The MC13144 and MC13158 are excellent solutions for a stable OOK receiver to fit part 15 applications such as keyless entry and security systems where high reliability and performance is essential. High performance attributes have been demonstrated and can be successfully integrated into a low-cost OOK communication system.

The varactor-controlled LC oscillator is capable of tuning over a suitable frequency range at low-supply voltage. Driving the VCO with the AFC network provides compensation for expected transmitter carrier drift. This overcomes the need for an expensive crystal-controlled transmitter/receiver system. Narrow band filters improve selectivity and assist in achieving the receiver's low sensitivity of -100 dBm. With only three ICs and a minimum number of external components, the low-cost objective is met.

The MC13176 offers a versatile UHF PLL transmitter using few external components and exceeds the performance criteria needed to adhere to the FCC regulations. It also fits manufacturing cost goals.

Both RF components interface well with the MC68HC705J1A MCU to provide more robust and dependable data recovery which ensures error-free switching of remote devices.

References

- [1] *Code of Federal Regulations, Title 47*. U.S. Government Printing Office, Washington, DC, 1992, Part 15, § 15.231.
- [2] *VHF – 2.0 GHz Low Noise Amplifier Advance Information*; document order number MC13144/D; Motorola, Inc.
- [3] *Wideband FM IF Subsystem for Dect and Digital Applications*, document order number MC13158/D; Motorola, Inc.
- [4] *UHF FM/AM Transmitter*, document order number MC13176/D; Motorola, Inc.
- [5] *MC68HC/HRC/HSC/HSR705J1A Technical Data*; document order number MC68HC705J1A/D; Motorola, Inc.
- [6] *Small Signal Transistors, FETs, and Diodes*, Motorola document order number DL126/D.
- [7] Rhea, Randall W. *Oscillator Design and Computer Simulation*. Prentice Hall, Inc., Englewood Cliffs, NJ, 1990.
- [8] *General-Purpose Transistor, NPN Silicon*; document order number MMBT3904L/D; Motorola, Inc.
- [9] *600GCS-8519N Coil Specification*. Toko America, Inc., Mt. Prospect, IL.
- [10] *150-04J08S Coil Specification*, Coilcraft, Cary, IL.
- [11] Balanis, Constantine A. *Antenna Theory: Analysis and Design*. Wiley, NY, 1982, pp.169-184.
- [12] Yoder, David. *HC05 MCU Keypad Decoding Techniques Using the MC68HC705J1A*; document order number AN1239/D, Motorola, Inc.
- [13] George, Scott. *HC05 Software-Driven Asynchronous Serial Communication Techniques Using the MC68HC705J1A*; document order number AN1240/D; Motorola, Inc.
- [14] Sibigtroth, James M. *Understanding Small Microcontrollers*, document order number M68HC05TB/D; Motorola, Inc.

Code Listing

```

*****
* Transmit Microcode for a Low Power Wireless Remote Control Unit
*
* Revision 7.1.98.2
* Grayhill Keypad
* Decode two keypad inputs, activate transmitter and send a message
*
* code is the first keypad input . command is the second keypad input
*
*****

*** I/O Pin Equates:
serial_port equ $01 ; port used for serial port pins
status_port equ $00 ; port used for driving LED's.
noise equ 4 ; pin # for noise LED
frame equ 5 ; pin # for frame LED
rxd equ 0 ; pin # for receive data pin
txd equ 4 ; pin # for transmit data pin
xmt equ 5 ; transmitter enable
BAUD_SEL equ $08 ; BAUD_SEL 4MHz osc 2 MHz osc
; $04 19.2k 9600
; $08 9600 4800
; $10 4800 2400
; $20 2400 1200
; $40 1200 600
; $80 600 300

char org 0c0 ; start of RAM space
char rmb 1 ; data register for sci
count rmb 1 ; temp storage variable
length rmb 1 ; preamble counter
code rmb 1 ; debounced key output storage #1
command rmb 1 ; debounced key output storage #2
flag rmb 1 ; software flags
; bit 0 - first key input done flag

*****
* Start of Program Space
*****
*Start - Initializes MCU hardware and enables interrupts.
*****
org 300 ;
Start:
KeyPdInt_Init:
ldx #$00 ;
rsp ; reset stack pointer
lda #$0 ; set port A register to all zeroes
sta PORTA ;
sta DDRA ; set Port A direction as Inputs

```

```

sta      PORTB          ; set Port B register to all zeroes
lda      #$3F          ; set Port B direction as
                        ; bit 5 output (transmitter switch)
                        ; bit 4 output (serial data out)
                        ; bit 3 output (output to switch)
                        ; bit 2 output (output to switch)
                        ; bit 1 output (output to switch)
                        ; bit 0 output (output to switch)

sta      DDRB          ; implement direction bits on Port B
lda      #$0F          ; load the lower nibble of port B
                        ; so when a keypad button is pushed
                        ; a port A interrupt occurs

sta      PORTB
clr      PDRA          : ensure pulldowns on port a are enabled
CLI      : Allow interrupts - IRQ pin 19 is
                        ; hardwired to logic 1 (no interrupt
                        ; from this pin) waiting for an
                        ; interrupt from Port A bits

shutdown  STOP          ; stop to conserve power - waiting
                        ; for a keyboard interrupt
bra      start         ; for getting back to stop when RTI
                        ; comes back

*****
* Send_preamble - routine that sends out a character stream to the transmitter *
* Character string is 55 55 55 code command *
*****
Send_preamble sta      code
bclr     txd,serial_port ; ensure serial out is low
bset     xmt,serial_port ; turn on the transmitter and wait for
                        ; stable frequency
                        ; generation

lda      #$05          ; load 5 millisecond constant
jsr      DelaymS2_Body ; go to delay routine

*
* *****
* * generate 500 microsecond logic 1 "front porch" *
* *****
bset     txd,serial_port ; ensure serial out is high
lda      #$50          ; generate a 500 microsecond
jsr      delay_13a     ; delay to trigger receiver

*
* *****
* * send three preamble characters of 55 hex *
* *****
lda      #$3           ; load count for sending
sta      length        ; number of 'preamble' char
alt_ones lda      #55   ; load preamble character
sta      char          ;
jsr      put_char      ; send the character in char
dec      length        ; decrement count
bne     alt_ones      ; go send another if not zero

```



```

* *****
* * route the address in 'code' to the routine that sends it out *
* *****

Send_code   lda     code           ; get the key-pad character
            sta     char           ; send out key-pad character
                                                ; insert a 12 cycle timing stall so
                                                ; receiver and transmitter routines take
                                                ; the same time between sent characters

            sta     char
            sta     char
            sta     char
            jsr     put_char        ; send address byte

* *****
* * route the command byte in "command" to the routine that sends it out *
* *****

            lda     command        ; get the command code
            sta     char
                                                ; insert a 12 cycle timing stall so
                                                ; receiver and transmitter routines
                                                ; take the same time between sent
                                                ; characters

            sta     char
            sta     char
            sta     char
            jsr     put_char        ; send command byte

* *****
* * turn off transmitter and initialize buffers for next time *
* *****

            bclr   txd,serial_port ; ensure serial out is zero
            bclr   xmt,serial_port ; turn off transmitter
            lda     #$0
            sta     code
            sta     command
            sta     flag
            rts

*****
* Routine from AN1240 written by Scott George *
*****

put_char    ldx     #9             ;[2] be sending 8 data bits
            clc                     ;[2] clear carry for start bit
put_data_bits bcc     send_0        ;[3] if carry<>0, then
            bset   txd,serial_port ;[5] send out a 1
            bra    jmp_bit          ;[3] finished sending a 1
send_0      bclr   txd,serial_port ;[5] else send a 0
            bra    jmp_bit          ;[3] finished sending a 0
jmp_bit     lda     #2*(BAUD_SEL-1)-1 ;[2] prepare for a 1 bit delay
            bsr     delay_13a       ;[13a+12] execute delay routine
            tsta                    ;[3] for timing purposes only
            ror     char            ;[5] get next data bit to send

```

AN1833

MOTOROLA

For More Information On This Product,
Go to: www.freescale.com

33

```

    decx                                ;[3] one bit sent, so dec count
    bne    put_data_bits                ;[3] loop if more bits to send

put_stop_bit  nop                      ;[2] for timing purposes only
             bset    txd,serial_port    ;[5] send out a one
             lda     #2*(BAUD_SEL-1)    ;[2] prepare for a 1 bit delay
             bsr     delay_13a          ;[13a+12] execute delay routine
             rts     ;[6] exit (put_char)

```

```

*****
* Delay routine from AN1240  written by Scott George
*****

```

```

delay_13a    nop                      ;[2] this is a 13-cycle loop
             nop                      ;[2]
             tsta    ;[3]
             deca    ;[3] decrement loop count
             bne    delay_13a          ;[3] loop if count not zero
             rts     ;[6] exit (delay_13a*)

```

```

*****
* Delay routine from AN1240  written by Scott George
*****

```

```

DelaymS2_Body:                                ;JSR EXT to get here        6
DelaymS2010  ldx     #$F8                    ;Load delay into X        2--\
DelaymS2020  decx   ; Decrement delay        3-\ |
             nop    ; burn 2 bus cycles      2 | |
             bne    DelaymS2020              ; Branch if not done      3- / |
             stx    COPR                      ;Service the WDOG         5 |
             ;Note that X will
             ;always be zero here
             brn    *                          ;Burn 3 bus cycles        3 |
             deca   ;decrement # of mS       3 |
             bne    DelaymS2010              ;branch if not done      3-- /
DelaymS2030  rts     ;return

```

```

*****
* Original Routine from AN1239 written by David Yoder and modified for use in
* A low-power Wireless Remote Control Transmitter and Receiver
* IRQ Interrupt Service Routine
*
* This is the external interrupt service routine. Both the external
* interrupt pin IRQ_ and the keypad interrupts use this routine.
* Note that in this version, any interrupt is interpreted as having only a keypad
* source
*****

```

```

KeyPdInt_Isr:                                ; Any decoding of external interrupts
                                             ; should be done here.
                                             ; The external and keypad interrupt share
                                             ; this vector.

KeyPdInt_Isr010:
    jsr    KeyPad_Body                      ;See if a key is pressed
    beq    KeyPdInt_Isr090                  ;If no key down, return to save power

```

```

        lda    #$4                ;Debounce key for 4mS
        jsr    DelaymS2_Body     ;Jump to delay routine
        jsr    KeyPad_Body       ;Get the keypress
KeyPdInt_Isr020:
        beq    KeyPdInt_Isr090   ;If no key down, return
                                   ;no key down = 00 in acu
KeyPdInt_Isr030:
        brset  first,flag,get2nd ; branch if first key seen
        sta    code              ; store address code
        bset   first,flag        ; set first key flag
        bra    KeyPdInt_Isr080   ; go wait for key release
get2nd   sta    command          ; store command byte
        jsr    Send_preamble     ;go send preamble & code

KeyPdInt_Isr080:
        jsr    KeyPad_Body       ; go check if the key has been released
        beq    KeyPdInt_Isr090   ; no key pressed so exit
        bra    KeyPdInt_Isr080   ; else wait for key release

KeyPdInt_Isr090:
        lda    #!10              ;Delay 10 mS
        jsr    DelaymS2_Body     ;Debounce the release
        bset   IRQR,ISCR         ;Clear any interrupt requests
                                   ; generated due to key bounce
        bclr   xmt,serial_port   ; turn off the transmitter
        rti                      ;Return from Interrupt (KeyPdInt_Isr)
                                   ;Interrupts can happen in any code in
                                   ; the main routine after this ISR has
                                   ; been called once.
                                   ;Remember this when changing the main
                                   ; routine!
*****
* This keypad decode routine is from AN1239 written by David Yoder      *
*                                                                           *
* KeyPad_Body                                                             *
*                                                                           *
* This subroutine decodes a 4x4 matrix keypad on port B.                 *
*                                                                           *
*****

KeyPad_Body:                                ;Load X with the offset of the last
                                             ;entry in the table
KeyPad010:
        ldx    #{KeyPad_Table_Top - KeyPad_Table}
        lda    portb              ;Get value in port B
        and   #$f0               ;Do not allow high nibble to change
        ora   KeyPad_Table+1,x    ;Get key decode value from table
        sta   portb              ;Write to Port

        lda    porta             ;Get value in port A
        and   #$0F               ;Throw out columns to read only rows
        cmp   KeyPad_Table,x     ;See if high nibble bit was pulled low
        beq   KeyPad030          ;If key found, branch
        decx                      ;Decrement X thrice to point to

```

AN1833

Application Note

```

                                ; next value in table
                                decx
                                decx
                                bpl    KeyPad010    ;If not below bottom of table
                                                ; try again.
                                ldx    #$00        ;A key was not decoded, so:
                                bra    KeyPad035    ;Return with null character

KeyPad030:
                                lda    KeyPad_Table+2,x    ;Load key code into Acc.
                                tax                                ;Store in X for now.

KeyPad035:
                                lda    portb    ;'Help' the pulldowns by driving the
                                and    #$F0        ; lines low. This minimizes current
                                sta    portb    ; draw while debouncing.

                                txa                                ;Get result back to Acc
                                tsta           ;Set the flags so calling routine
                                                ; can use them for decisions.

KeyPad040    rts                                ;Return with result value in Acc

```

```

;Table of keypad decode values and codes.
;Fill in your own key codes. Codes must be 1
; byte each. Currently row 1 col 1 = 0, which
; duplicates no key found. This is a result
; of limiting the codes to 4 bits for display
; on PA[4..7]

```

```

                                ; Row    Column
KeyPad_Table:
                                DB    $01,$01,$F1    ; PA0    PB0
                                DB    $01,$02,$F2    ; PA0    PB1
                                DB    $01,$04,$F3    ; PA0    PB2
                                DB    $01,$08,$FA    ; PA0    PB3
                                DB    $02,$01,$F4    ; PA1    PB0
                                DB    $02,$02,$F5    ; PA1    PB1
                                DB    $02,$04,$F6    ; PA1    PB2
                                DB    $02,$08,$FB    ; PA1    PB3
                                DB    $04,$01,$F7    ; PA2    PB0
                                DB    $04,$02,$F8    ; PA2    PB1
                                DB    $04,$04,$F9    ; PA2    PB2
                                DB    $04,$08,$FC    ; PA2    PB3
                                DB    $08,$01,$FF    ; PA3    PB0
                                DB    $08,$02,$FE    ; PA3    PB1
                                DB    $08,$04,$FF    ; PA3    PB2
KeyPad_Table_Top    DB    $08,$08,$FD    ; PA3    PB3

```

```

#include 'H705J1A.FRK'                                ;Include the equates for the HC705J1A

```

```

                                org    MOR
                                fcb    06                                ;Enable Port A Interrupts
                                                ;If used on a mask rom part,
                                                ; be sure to specify this option.
                                                ;Enable level sensitivity on IRQs
                                                ; SOSCD = Short Oscillator delay
                                                ; enable

```

```

; EPMSEC = EPROM Security
; OSCRES = Oscillator Parallel
; Resistor
; SWAIT = Stop Instruction Mode
; SWPDI = Port Pulldown Inhibit
; PIRQ = Port A Interrupt Function
; LEVEL = IRQ Edge Sensitivity
; COPEN = COP Watchdog enable
;Software pull down inhibit = off
;Stop = Halt disabled
;OSC parallel resistor disabled
;EPROM security off
;Short OSC recovery disabled

```

```

org     RESET
fdb     Start
org     IRQ_INT
fdb     KeyPdINT_Isr

```

```

*****
* Receiver Microcode for a Low Power Wireless Remote Control Unit *
* REVISION 7.9.98.2 *
* *
*****
* Full Functional Description of Routine Design: *
* Program flow: *
* Main/Reset: Call init to intialize port pins and interrupts *
* Clean up the buffers *
* *
*****

*****
* Part Specific Framework Include Section *
*****
#include 'H705J1A.FRK' ; Include the equates for the
                       ; HC705J1A so all labels can be found.

*****
* *
* Equates and RAM Storage *
* *
*****
*** I/O Pin Equates:
serial_port equ $01 ; port used for serial port pins
status_port equ $00 ; port used for driving LED's.
noise equ 4 ; pin # for noise LED
frame equ 5 ; pin # for frame LED
rx equ 4 ; pin # for receive data pin
tx equ 1 ; pin # for transmit data pin
passflag equ 7 ; timer monitor bit

*** Program Constant Equates: ; Baud rate select table:

```

Application Note

```

BAUD_SEL      equ      $08                ; BAUD_SEL      4MHz osc      2MHz osc
                                           ; $04 19.2 k 9600
                                           ; $08      9600      4800
                                           ; $10 4800      2400
                                           ; $20 2400      1200
                                           ; $40 1200       600
                                           ; $80   600       300

*** RAM variable allocation:
      org      0C0
char      rmb      1                ; incoming data register
count     rmb      1                ; temp storage variable
cmpr      rmb      1                ; compare register
xcnt      rmb      1                ; counter
length    rmb      1                ; index pointer storage
buffer     rmb      8                ; receiver buffer
flag       rmb      1                ; flag bits - bit 0 = got a 55
*****
*
*
*
      org      300                ; start at the top of ROM
main      rsp
          ldx      #$0                ; reset the stack pointer
          jsr      init                ; initialize port pins & ints
          lda      #$4                ; load bit counter to 3
          sta      count
Wait_for_data brset   rxd,PORTB,front_porch ; branch if incoming data =1
          inc      xcnt                ; increment a count
          bcc      Wait_for_data       ; check for incoming data
          lda      #$00                ; carry set so clear the count
look_again sta      xcnt                ; and go back to examining data
          bra      Wait_for_data
*****
* frontporch -takes a 4-bit sample and looks for logic 1
*****
front_porch equ      *
          jsr      get_bit                ;[39] sample data bit
          rora                ;[3] noise bit -> carry
          rorx                ;[3] carry -> noise data reg
          rora                ;[3] filtered data bit -> carry
          ror      char                ;[5] carry -> char
          lda      #2*(BAUD_SEL-3)      ;[2] prepare for 1 bit delay
          jsr      delay_13a            ;[13a+12] execute delay routine
          tsta                ;[3] for timing purposes only
          dec      count                ;[5] bit received, dec count
          bne      front_porch          ;[3] loop if more bits to get
          lda      #$f0                ; check for bit value received
          cmp      char                ; looking for 4 one bits
          beq      get_data            ; four logic 1 bits received - go wait
                                           ; for incoming data
          jmp      main                ; invalid frontporch -restart

```

Freescale Semiconductor, Inc.

```

*****
* get_data - the routine that acquires data and puts it into the receive buffer.  *
* A timer interrupt is the expected exit path.  timer interval is 8.2 msec      *
*****
get_data      lda      #$1C                ; initialize timer register
              STA      TSCR                ; and allow interrupts
              cli      ; clear I bit in CCR
              lda      #$0                ; initialize the index
              sta      length              ; store in memory
main_loop     jsr      get_char            ; receive one byte of data from rxd pin
              lda      char                ; get the current character
              ldx      length              ; load buffer index
              sta      buffer,x           ; store character in recv buffer
              lda      #$3                ; check for buffer full
              cmp      length              ; is count 3? (buffer full)

waiting_for_int beq      waiting_for_int    ; wait here for interrupt if receive
              ; buffer is full

*          *****
*          * waiting for timer interrupt- expected exit point - see RTI_int *
*          *****
              inc      length              ; increment buffer pointer
              bra      main_loop           ; go get another byte
*****
**
***
**** Entry point for timer interrupt routine
***
**
*****
Timer_SVR     equ      *                  ;
RTI_int       equ      *                  ; Real Time Interrupt routine
              sei      ; disable interruptss
              lda      #$0C               ; clear timer overflow flag
              ; clear RTI flag
              ; Timer overflow disable
              ; Real Time Interrupt disable
              ;
              sta      TSCR
check_msg_forma lda     #$0                ; initialize the index
              sta      length              ; in location length
              sta      flag                ; clear all flags
              ldx      length              ; and load the index register
              lda      #$55               ; looking for a 55
              sta      char
look          lda      buffer,x            ; get a buffer character
              cmp      char                ; check if it's a 55
              beq      got_one              ; branch if a 55
next         incx
              inc      length              ; looked for all possible 55s?
              lda      #$3                ; in the first three buffer
              cmp      length              ; locations
              beq      done                ; branch if so
              bra      look                ; go back and look some more

```

Application Note

```

got_one      brset   0,flag,prev55      ; branch if saw a 55 previously
             bset    0,flag            ; set the flag
             bra     next              ; go look for another 55
prev55       ldx     #$3                ; get code character in buffer
             lda     #$f5              ; compare for address desired - this
value changes
             cmp     buffer,x          ;
             beq     toggle            ; go execute the command byte if address
             ; byte match
             lda     #$fc              ; compare for broadcast address
             cmp     buffer,x          ;
             beq     toggle            ; go execute the command byte
             ; if a broadcast address match
done         jmp     main              ; else- go reset everything and wait for
             ; the front porch
    
```

```

*****
* command byte checking
*****
    
```

```

toggle       ldx     #$4                ; set index to command byte
             lda     #$FA              ; check for an on command
             cmp     buffer,x          ;
             beq     turnon            ; branch if turn on command
             lda     #$FB              ; compare for turn off command
             cmp     buffer,x          ;
             beq     turnoff           ; branch if turn off command
             bra     done              ; else invalid command so...

turnon       bset    5,portb           ; set the port bit
             bra     done              ; command executed so...

turnoff      bclr   5,portb           ; reset the port bit
             bra     done              ; command executed so ...
    
```

```

*****
* init - initialize port pins, disable interrupts. Clear all buffers and flags *
*      called by main *
* *
* input cond.      - none *
* output cond.    - Port B bit 5= output , RXD = input *
* stack used      - 0 bytes *
* variables used  - none *
*****
    
```

```

init         lda     #$0                ; all port a pins are inputs
             STA    DDRA                ; (all port a pins are grounded)
             lda     #$20              ; port b pin 5 output - to device to be
             ; turned on and off
             STA    DDRB                ; pin 4 input - data from the receiver
             lda     #$00              ; load ISCR to 00 - no external
             ; interrupts from IRQ Port A
             STA    ISCR
             lda     #$0C              ; load TSCR (timer Control) so 0= turn
             ; off RTIC= RTI enable,
             ; clear RTIFlag
    
```



```

STA      TSCR                ; C= RTI = enable, clear RTI Flag
lda      #$0                 ; clear buffers
sta      flag                ; clear 55 flag
sta      char                ; cleaar receiver memory location
sta      length              ; clear index counter
ldx      #$0
sta      buffer,x            ; clear receive buffer
incx                    ; location 0
sta      buffer,x
incx                    ; location 1
sta      buffer,x
incx                    ; location 2
sta      buffer,x
incx                    ; location 3
sta      buffer,x
rts

```

```

*****
* incoming/get_char - Routine from AN1240 written by Scott George *
* called by get_data *
* input cond. - RXD pin defined as an input pin *
* - expecting a preamble character of where four bits are logic 1 *
* - followed by a series of 55 55 55 fx fx *
* get_char - receive one byte of data from RXD pin; called by main *
* *
* input cond. - RXD pin defined as an input pin *
* output cond. - char contains received data; X,ACC undefined; *
* half carry = 1 (frame error occurred) or 0 (no frame error); *
* carry = 1 (noise and/or frame error occurred) or 0 (no noise) *
* stack used - 2 bytes *
* variables used - char: storage for received data (1 byte) *
* count: temporary storage (1 byte) *
* ROM used - 63 bytes *
*****

```

```

incoming:
get_char      lda      #8                ;[2] receiving 8 data bits
              sta      count            ;[4] store value into RAM
              clr     clrx              ;[3] used to store noise data

get_start_bit brclr   rxd,serial_port,*  ;[5] wait until rxd=1
              brset   rxd,serial_port,*  ;[5] wait for start bit
              lda      #BAUD_SEL-3      ;[2] prepare for 1/2 bit delay
              bsr     delay_13a         ;[13a+12] execute delay routine
              bsr     get_bit           ;[39] sample start bit
              lsra                    ;[3] noise bit -> carry;
              ; acc=filtered start bit
              bne     get_start_bit     ;[3] if false start, start over
              tsta                    ;[3] for timing purposes only
              tsta                    ;[3] for timing purposes only

              lda      #2*(BAUD_SEL-2)  ;[2] prepare for 1 bit delay
              bsr     delay_13a         ;[13a+12] execute delay routine

```

Application Note

```

get_data_bits bsr      get_bit          ;[39] sample data bit
              rora      ;[3] noise bit -> carry
              rorx     ;[3] carry -> noise data reg
              rora     ;[3] filtered data bit -> carry
              ror      char           ;[5] carry -> char
              lda      #2*(BAUD_SEL-3) ;[2] prepare for 1 bit delay
              bsr      delay_13a      ;[13a+12] execute delay routine
              tsta     ;[3] for timing purposes only
              dec      count          ;[5] bit received, dec count
              bne     get_data_bits   ;[3] loop if more bits to get

get_stop_bit  bsr      get_bit          ;[39] sample stop bit
              lsra     ;[3] noise bit -> carry
              ; acc=filtered stop bit
              sta      count          ;[4] store stop bit in count
              bcc     yes_noise       ;[3] if noise, then branch

              txa      ;[2] noise data -> acc
              eor     char           ;[3] XOR noise with char,
              beq     no_noise        ;[3] and if result=0,
              ; then no noise in data
              ; reception

yes_noise     lda      #$08           ;[2] set noise bit (half carry)
              add     #$08           ;[2] by adding $8 to $8

no_noise      lda      count          ;[3] retrieve stop data bit,
              coma    ;[3] complement it,
              lsra    ;[3] and shift it into carry
              ; for frame error bit
              rts      ;[6] exit (get_char)
    
```

```

*****
* Routine from AN1240 written by Scott George *
* get_bit - receive one bit of filtered data and noise info; *
* called by get_char and frontporch *
* *
* input cond. - RXD pin defined as an input pin *
* output cond. - ACC = 000000dn, where d = filtered data, n = noise info *
* stack used - 0 bytes *
* variables used - none *
* ROM used - 17 bytes *
*****
    
```


```

get_bit      clra      ;[3] used to add sampled bits
              brset   rxd,serial_port,samp_1 ;[5] sample 1st bit into carry
samp_1 adc   #0        ;[3] add it to acc
              brset   rxd,serial_port,samp_2 ;[5] sample 2nd bit into carry
samp_2 adc   #0        ;[3] add it to acc
              brset   rxd,serial_port,samp_3 ;[5] sample 3rd bit into carry
samp_3      adc      #0        ;[3] add it to acc
              rts      ;[6] exit (get_bit)
    
```

```

*****
* Routine from AN1240 written by Scott George
* delay_13a - delay for 13*ACC + 12 cycles; called by get_char and front porch
*
* input cond.      - ACC set to appropriate value (13*ACC + 12 cycles)
* output cond.     - ACC = 0
* stack used      - 0 bytes
* variables used- none
* ROM used        - 7 bytes
*****
delay_13a      nop                ;[2] this is a 13-cycle loop
               nop                ;[2]
               tsta               ;[3]
               deca               ;[3] decrement loop count
               bne    delay_13a   ;[3] loop if count not zero
               rts                ;[6] exit (delay_13a)
*****
*
*           MOR Bytes Definitions for the Main Routine
*
*****
               org    MOR
               fcb    $00
*****
*
*           Interrupt and Reset vectors for Main Routine
*
*****
               org    RESET                ; When reset occurs, go to routine main
               fdb    main
               org    Timer_INT            ; When interrupt occurs, go to routine
               fdb    Timer_SVR            ; Timer_SVR

```

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Motorola data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

How to reach us:

USA/EUROPE/Locations Not Listed: Motorola Literature Distribution; P.O. Box 5405, Denver, Colorado 80217. 1-303-675-2140 or 1-800-441-2447

JAPAN: Motorola Japan Ltd.; SPS, Technical Information Center, 3-20-1, Minami-Azabu, Minato-ku, Tokyo 106-8573 Japan. 81-3-3440-3569

ASIA/PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Centre, 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.
852-26668334

Technical Information Center: 1-800-521-6274

HOME PAGE: <http://www.motorola.com/semiconductors/>



MOTOROLA

© Motorola, Inc., 2000

AN1833/D

**For More Information On This Product,
Go to: www.freescale.com**