ROHM
SEMICONDUCTOR

Structure	Silicon Monolithic Integrated Circuit
Product Name	Step-up DC/DC converter for medium size LCD panel
Type	**BD6586MUV**
Features	High efficiency PWM step-up DC/DC converter (fsw=1MHz) High accuracy and good matching current driver 4ch Drive up to 6 in series × 4 strings in parallel =24white LEDs (*white LED Vf=4.0Vmax)

○Absolute maximum ratings (Ta=25 $^{\circ}$C)

Parameter	Symbol	Limits	Unit	Condition
Maximum applied voltage 1	VMAX1	7	V	VBAT, EN1, EN2, TRSW, PWM, TESTO, ISET, TEST
Maximum applied voltage 2	VMAX2	25	V	LED1, LED2, LED3, LED4,
Maximum applied voltage 3	VMAX3	30.5	V	SW
Maximum applied voltage 4	VMAX4	50.5	V	VDET
Power dissipation 1	Pd1	500	mW	*1
Power dissipation 2	Pd2	780	mW	*2
Power dissipation 3	Pd3	1510	mW	*3
Operating temperature range	Topr	-40 ~ +85	$^{\circ}$C	-
Storage temperature range	Tstg	-55 ~ +150	$^{\circ}$C	-

(*1) It will be reduced every 4.0mW/$^{\circ}$C (Ta>25 $^{\circ}$C) when it's not mounted on a heat radiation Board.
(*2) it will be reduced every 6.2mW/$^{\circ}$C (Ta>25 $^{\circ}$C) when It's not mounted on 1 layer board (ROHM Standard board) and Copper foil area 0mm^2
(*3) It will be reduced every 12.1mW/$^{\circ}$C (Ta>25 $^{\circ}$C) when it's mounted on 4 layer board (JEDEC Compliant board) and Copper foil area 6.28mm^2 on 1st layer and Copper foil area 5655.04mm^2. 2nd-4th layer.

○Operating conditions (Ta=-40 to +85 $^{\circ}$C)

Parameter	Symbol	Rating			Unit	Condition
		Min.	Typ.	Max.		
Supply voltage	VBAT		2.7 ~ 5.5		V	

This product isn't designed to protect itself against radioactive rays.

ROHM
SEMICONDUCTOR

○Electrical Characteristics

(Unless otherwise noted, VBAT=3.6V, Ta = +25 ^{o}C)

Parameter	Symbol	Spec			Unit	Condition
		Min.	Typ.	Max.		
EN1, EN2, PWM Pin						
Low Input Voltage range	VthL	0	-	0.4	V	
High Input Voltage range	VthH	1.4	-	5.5	V	
Input current	Iin	-	8.3	16.0	µA	Input voltage=2.5V
UVLO						
Under Voltage Lock Out	UVLO	2.05	2.35	2.65	V	VBAT falling edge
Switching Regulator						
Quiescent Current	Iq	-	0.1	2.0	µA	EN1=EN2=PWM=0V
Current Consumption	Idd	-	2.2	4.6	mA	VDET=0V,ISET=24kΩ
LED Control voltage	VLED	0.4	0.5	0.6	V	
Over Current Limit	Ocp	1.1	1.5	2.5	A	*1
SBD Open Protect	Sop	-	-	0.1	V	Detect voltage of VDET pin
Switching frequency	fSW	0.7	1.0	1.3	MHz	
Duty cycle limit	Duty	91	95	99	%	LED1-4=0.3V
Over Voltage Limit	Ovl	25.0	25.5	26.0	V	LED1-4=0.3V
SW Transistor On Resistance	RSW	-	0.24	0.32	Ω	Isw=100mA
Current driver						
LED maximum current	ILMAX	-	-	25	mA	
LED current accuracy	ILACCU	-	-	±5	%	ILED=20mA
LED current matching	ILMAT	-	-	±3	%	▪Each LED current/Average (LED1- 4 current) ▪ILED=20mA
ISET voltage	Iset	0.5	0.6	0.7	V	
LED current limiter	ILOCP	35	60	90	mA	ISET resistance 4.7kΩ LED1- 4 =0.5V
LED Terminal Over Voltage Protect	LEDOVP	10.0	11.5	13.0	V	EN1=EN2=PWM=2.5V

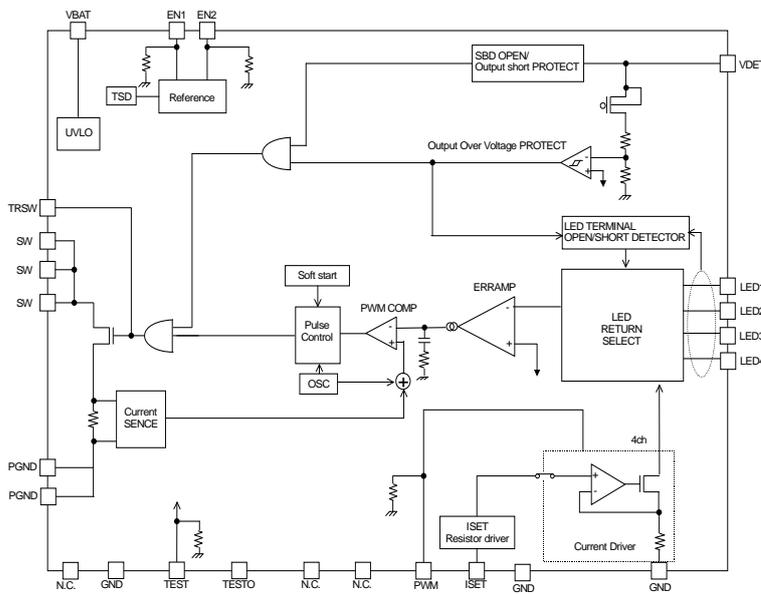*1. This parameter is tested with dc measurement.

○Package outline drawing (Unit : mm)

Type

D6586

1PIN MARK

LOT No.

4.0±0.1
4.0±0.1

1.0MAX

0.08S

2.4±0.1
2.4±0.1
0.4±0.1
C0.2
0.75
0.5
0.25 +0.05 -0.04
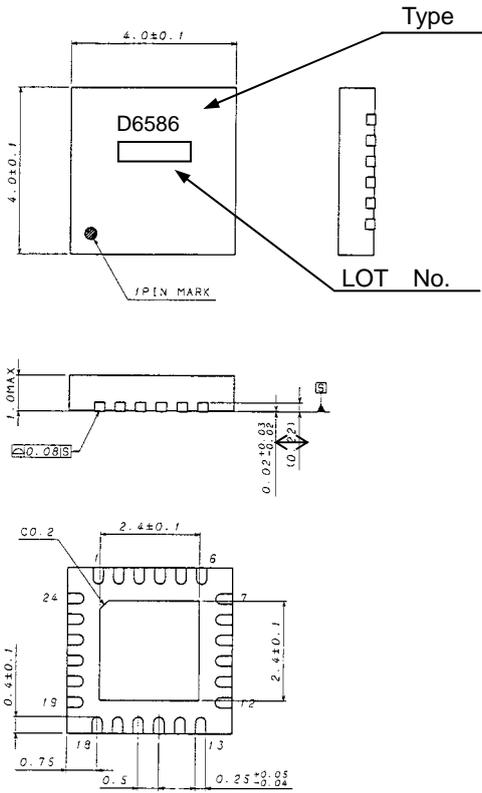
VQFN024V4040

○Terminals

PIN	PIN Name
1	VBAT
2	EN1
3	EN2
4	GND
5	PWM
6	ISET
7	GND
8	LED1
9	LED2
10	GND
11	LED3
12	LED4
13	TEST
14	TESTO
15	N.C.
16	SW
17	SW
18	SW
19	VDET
20	N.C.
21	PGND
22	PGND
23	N.C.
24	TRSW

○Block diagram

○Cautions on use

(1) Absolute Maximum Ratings

An excess in the absolute maximum ratings, such as supply voltage, temperature range of operating conditions, etc., can break down devices, thus making impossible to identify breaking mode such as a short circuit or an open circuit. If any special mode exceeding the absolute maximum ratings is assumed, consideration should be given to take physical safety measures including the use of fuses, etc.

(2) Power supply and GND line

Design PCB pattern to provide low impedance for the wiring between the power supply and the GND lines. Pay attention to the interference by common impedance of layout pattern when there are plural power supplies and GND lines. Especially, when there are GND pattern for small signal and GND pattern for large current included the external circuits, please separate each GND pattern. Furthermore, for all power supply terminals to ICs, mount a capacitor between the power supply and the GND terminal. At the same time, in order to use a capacitor, thoroughly check to be sure the characteristics of the capacitor to be used present no problem including the occurrence of capacity dropout at a low temperature, thus determining the constant.

(3) GND voltage

Make setting of the potential of the GND terminal so that it will be maintained at the minimum in any operating state. Furthermore, check to be sure no terminals are at a potential lower than the GND voltage including an actual electric transient.

(4) Short circuit between terminals and erroneous mounting

In order to mount ICs on a set PCB, pay thorough attention to the direction and offset of the ICs. Erroneous mounting can break down the ICs. Furthermore, if a short circuit occurs due to foreign matters entering between terminals or between the terminal and the power supply or the GND terminal, the ICs can break down.

(5) Operation in strong electromagnetic field

Be noted that using ICs in the strong electromagnetic field can malfunction them.

(6) Input terminals

In terms of the construction of IC, parasitic elements are inevitably formed in relation to potential. The operation of the parasitic element can cause interference with circuit operation, thus resulting in a malfunction and then breakdown of the input terminal. Therefore, pay thorough attention not to handle the input terminals, such as to apply to the input terminals a voltage lower than the GND respectively, so that any parasitic element will operate. Furthermore, do not apply a voltage to the input terminals when no power supply voltage is applied to the IC. In addition, even if the power supply voltage is applied, apply to the input terminals a voltage lower than the power supply voltage or within the guaranteed value of electrical characteristics. And, as the unused input terminals may make unstable state occur in the internal circuit, please connect them to I/O GND.

(7) External capacitor

In order to use a ceramic capacitor as the external capacitor, determine the constant with consideration given to a degradation in the nominal capacitance due to DC bias and changes in the capacitance due to temperature, etc.

(8) Thermal shutdown circuit (TSD)

When junction temperatures become 175°C (typ) or higher, the thermal shutdown circuit operates and turns a switch OFF.   The thermal shutdown circuit, which is aimed at isolating the LSI from thermal runaway as much as possible, is not aimed at the protection or guarantee of the LSI.   Therefore, do not continuously use the LSI with this circuit operating or use the LSI assuming its operation.

(9) Thermal design

Perform thermal design in which there are adequate margins by taking into account the permissible dissipation (Pd) in actual states of use.

(10) DC/DC converter

Please select the low DCR inductors to decrease power loss for DC/DC converter.

Notes

No copying or reproduction of this document, in part or in whole, is permitted without the consent of ROHM Co.,Ltd.

The content specified herein is subject to change for improvement without notice.

The content specified herein is for the purpose of introducing ROHM's products (hereinafter "Products"). If you wish to use any such Product, please be sure to refer to the specifications, which can be obtained from ROHM upon request.

Examples of application circuits, circuit constants and any other information contained herein illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.

Great care was taken in ensuring the accuracy of the information specified in this document. However, should you incur any damage arising from any inaccuracy or misprint of such information, ROHM shall bear no responsibility for such damage.

The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM and other parties. ROHM shall bear no responsibility whatsoever for any dispute arising from the use of such technical information.

The Products specified in this document are intended to be used with general-use electronic equipment or devices (such as audio visual equipment, office-automation equipment, communication devices, electronic appliances and amusement devices).

The Products specified in this document are not designed to be radiation tolerant.

While ROHM always makes efforts to enhance the quality and reliability of its Products, a Product may fail or malfunction for a variety of reasons.

Please be sure to implement in your equipment using the Products safety measures to guard against the possibility of physical injury, fire or any other damage caused in the event of the failure of any Product, such as derating, redundancy, fire control and fail-safe designs. ROHM shall bear no responsibility whatsoever for your use of any Product outside of the prescribed scope or not in accordance with the instruction manual.

The Products are not designed or manufactured to be used with any equipment, device or system which requires an extremely high level of reliability the failure or malfunction of which may result in a direct threat to human life or create a risk of human injury (such as a medical instrument, transportation equipment, aerospace machinery, nuclear-reactor controller, fuel-controller or other safety device). ROHM shall bear no responsibility in any way for use of any of the Products for the above special purposes. If a Product is intended to be used for any such special purpose, please contact a ROHM sales representative before purchasing.

If you intend to export or ship overseas any Product or technology specified herein that may be controlled under the Foreign Exchange and the Foreign Trade Law, you will be required to obtain a license or permit under the Law.

Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

http://www.rohm.com/contact/