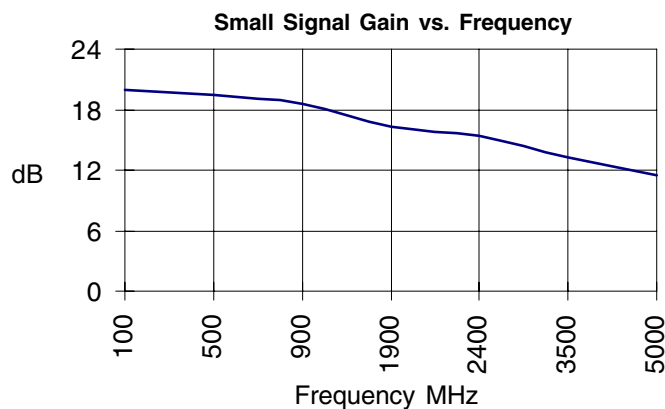


Product Description

Stanford Microdevices' SGA-5486 is a high performance cascadeable 50-ohm amplifier designed for operation at voltages as low as 3.5V. This RFIC uses the latest Silicon Germanium Heterostructure Bipolar Transistor (SiGe HBT) process featuring 1 micron emitters with F_T up to 65 GHz.

This circuit uses a darlington pair topology with resistive feedback for broadband performance as well as stability over its entire temperature range. Internally matched to 50 ohm impedance, the SGA-5486 requires only DC blocking and bypass capacitors for external components.



Electrical Specifications at $T_a = 25^\circ\text{C}$

Symbol	Parameters: Test Conditions: $Z_0 = 50 \text{ Ohms}$, $f = \text{DC-2400 MHz}$		Units	Min.	Typ.	Max.
P_{1dB}	Output Power at 1dB Compression	$f = 850 \text{ MHz}$ $f = 1950 \text{ MHz}$	dBm dBm		17.0 15.0	
S_{21}	Small Signal Gain	$f = \text{DC-1000 MHz}$ $f = 1000\text{-}2000 \text{ MHz}$ $f = 2000\text{-}5000 \text{ MHz}$	dB dB dB	17.5	19.7 17.3 13.5	
S_{12}	Reverse Isolation	$f = \text{DC-1000 MHz}$ $f = 1000\text{-}2000 \text{ MHz}$ $f = 2000\text{-}5000 \text{ MHz}$	dB dB dB		22.5 23.0 18.0	
S_{11}	Input VSWR	$f = \text{DC-5000 MHz}$	-		1.50:1	
S_{22}	Output VSWR	$f = \text{DC-5000 MHz}$	-		1.50:1	
IP_3	Third Order Intercept Point	$f = 850 \text{ MHz}$ $f = 1950 \text{ MHz}$	dBm dBm		32.0 28.0	
NF	Noise Figure	$f = \text{DC-1000 MHz}$ $f = 1000\text{-}2400 \text{ MHz}$	dB dB		3.0 3.5	
T_D	Group Delay	$f = 1000 \text{ MHz}$	pS		121.0	
V_D	Device Voltage		V	3.1	3.5	3.9
I_D	Device Current		mA		60.0	

The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems. Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

SGA-5486

DC-2400 MHz Silicon Germanium HBT Cascadeable Gain Block



Product Features


- DC-2400 MHz Operation
- Single Voltage Supply
- High Output Intercept: +32.0dBm typ. at 850 MHz
- Low Current Draw: 60mA at 3.5V typ.
- Low Noise Figure: 3.0dB typ. at 850 MHz

Applications


- Oscillator Amplifiers
- PA for Low Power Applications
- IF/ RF Buffer Amplifier
- Drivers for CATV Amplifiers

Parameter	Specification				Test Condition
	Min	Typ.	Max.	Unit	
Bandwidth Frequency Range	DC		2400	MHz	T= 25C
Device Bias Operating Voltage Operating Current		3.5 60.0		V mA	T= 25C
500 MHz Gain Noise Figure Output IP3 Output P1dB Input Return Loss Isolation		19.5 3.0 31.6 17.0 19.5 22.6		dB dB dBm dBm dB dB	T= 25C
850 MHz Gain Noise Figure Output IP3 Output P1dB Input Return Loss Isolation		18.8 3.1 32.0 17.0 13.3 22.9		dB dB dBm dBm dB dB	T= 25C
1950 MHz Gain Noise Figure Output IP3 Output P1dB Input Return Loss Isolation		16.3 3.6 28.0 15.0 13.7 22.9		dB dB dBm dBm dB dB	T= 25C
2400 MHz Gain Noise Figure Output IP3 Output P1dB Input Return Loss Isolation		15.4 3.7 26.0 13.6 16.8 22.0		dB dB dBm dBm dB dB	T= 25C


The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems.
Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

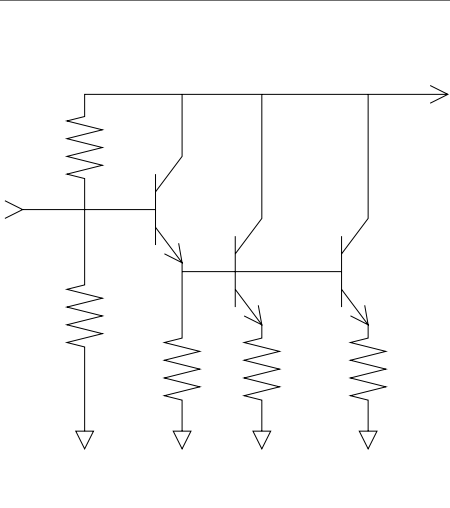Pin #	Function	Description	Device Schematic
1	RF IN	RF input pin. This pin requires the use of an external DC blocking capacitor chosen for the frequency of operation.	
2	GND	Connection to ground. Use via holes for best performance to reduce lead inductance as close to ground leads as possible.	
3	RF OUT/ BIAS	RF output and bias pin. DC voltage is present on this pin, therefore a DC blocking capacitor is necessary for proper operation.	
4	GND	Sames as Pin 2	






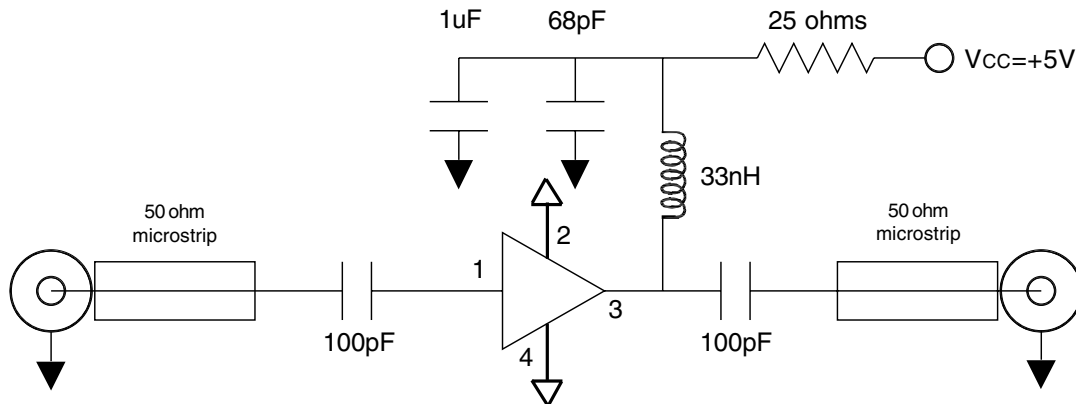
Application Schematic for +5V Operation at 900 MHz








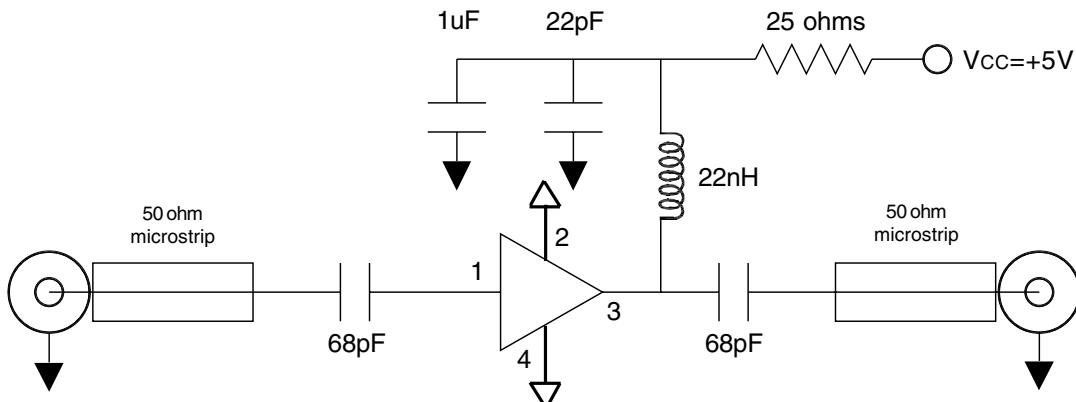
Application Schematic for +5V Operation at 1900 MHz









The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems. Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

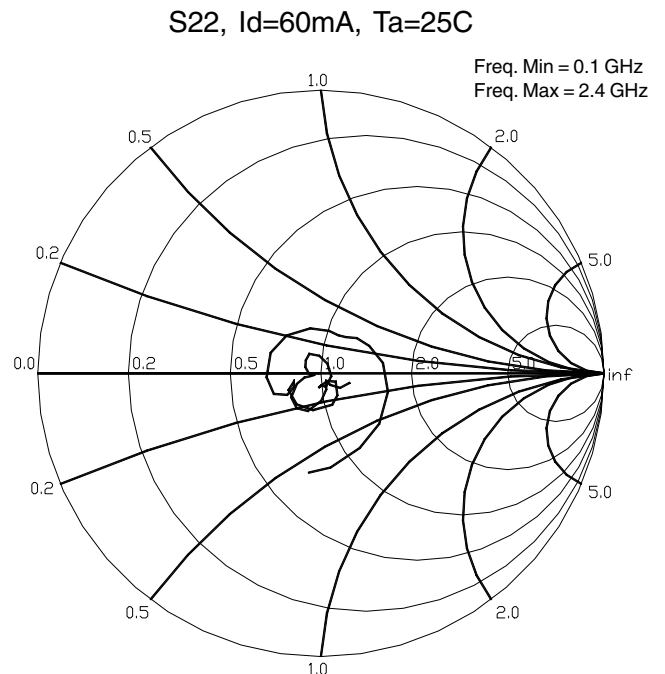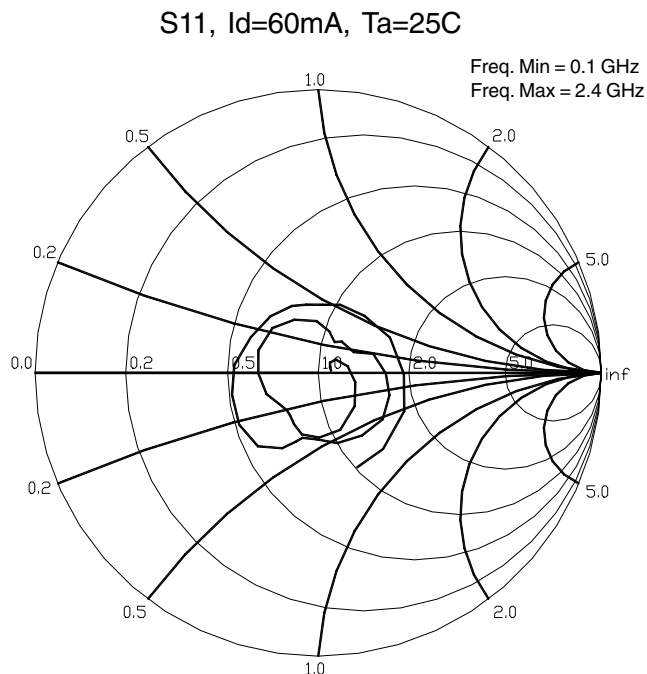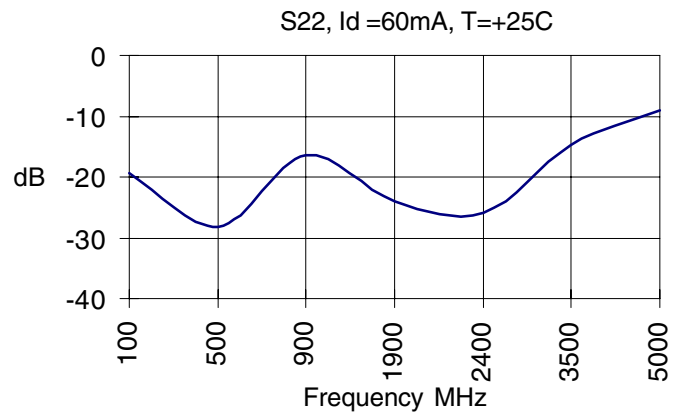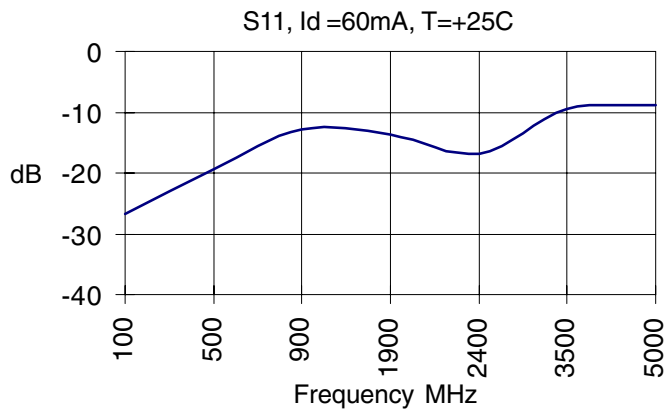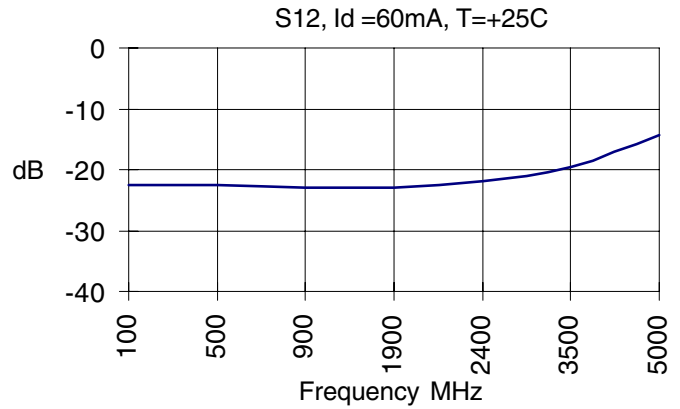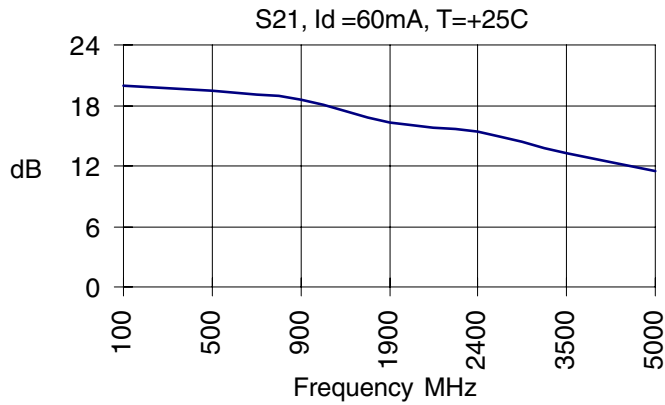

The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems. Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

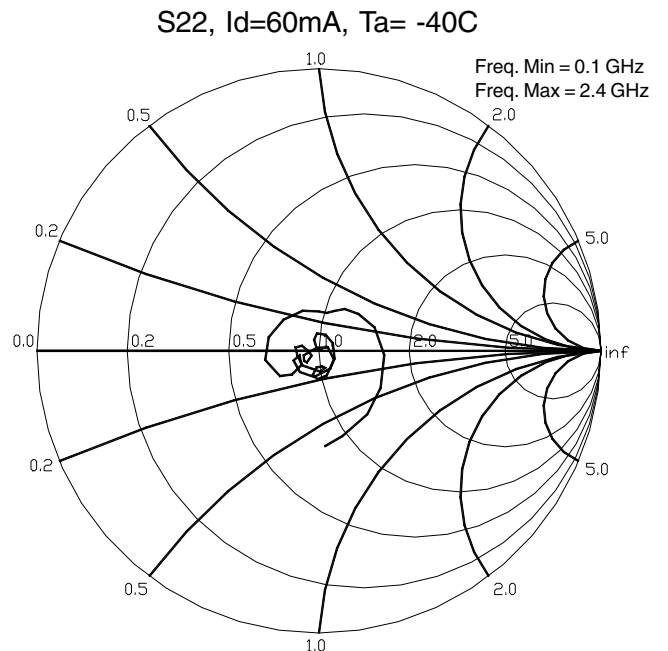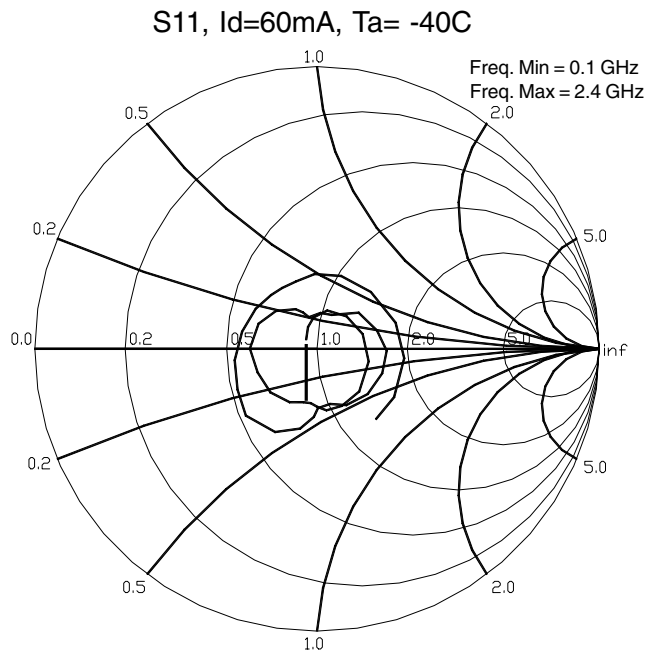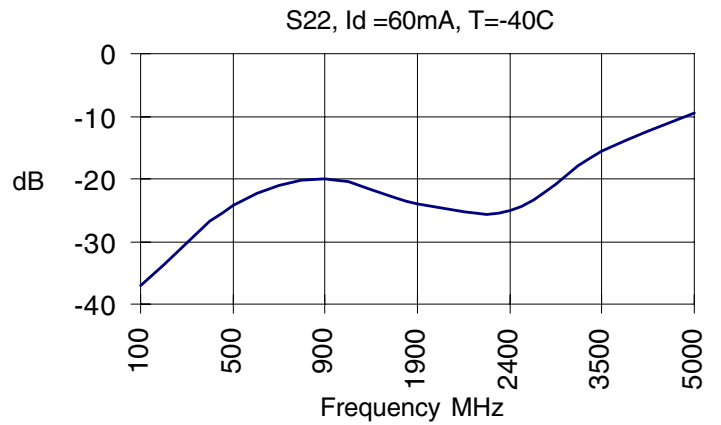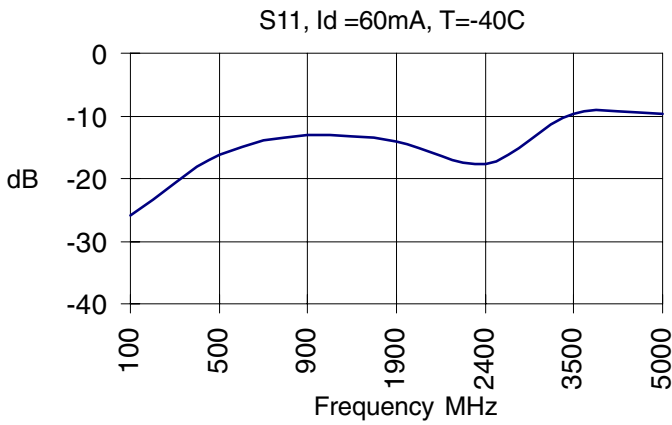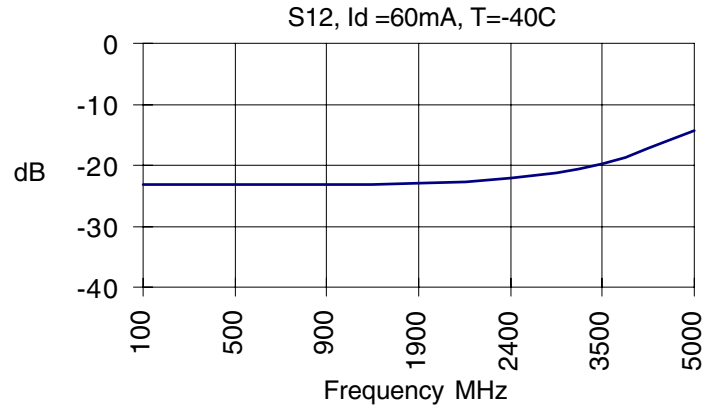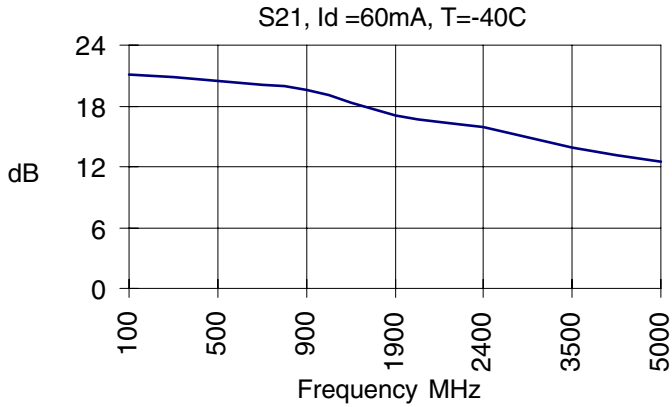

The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems. Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

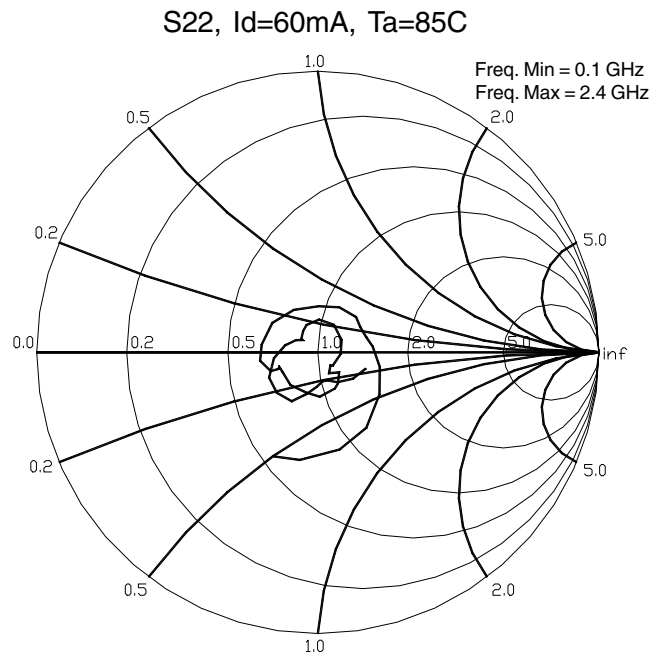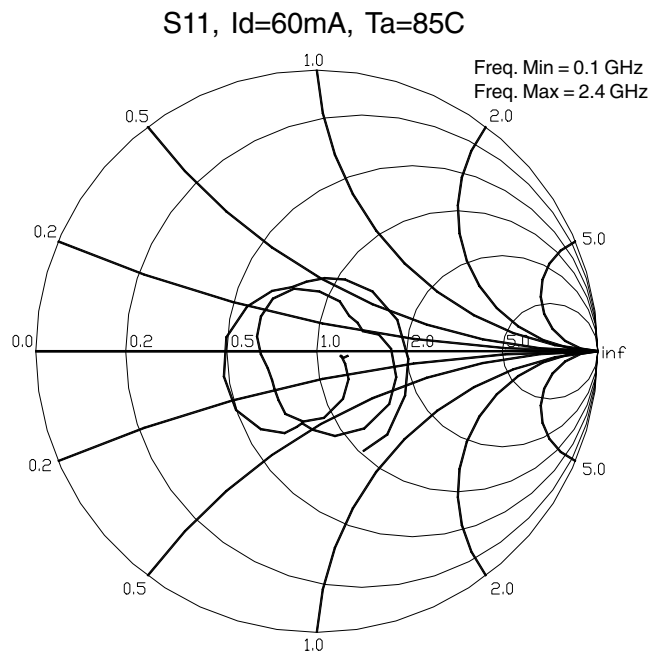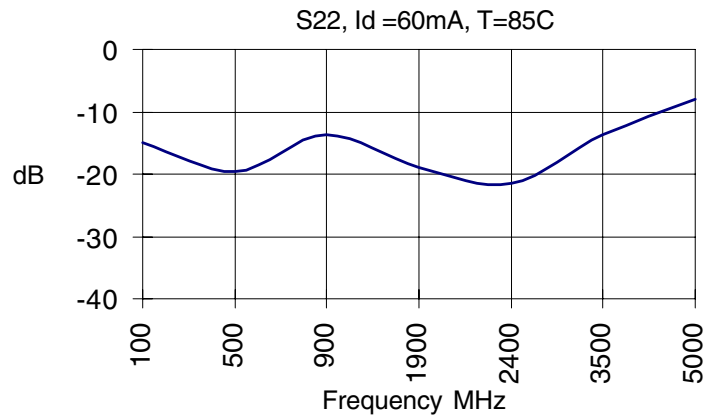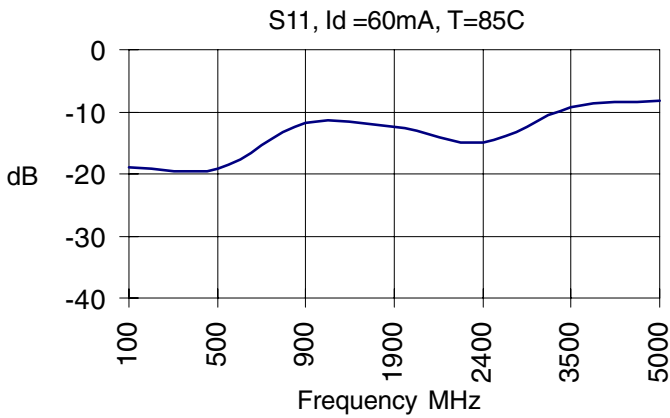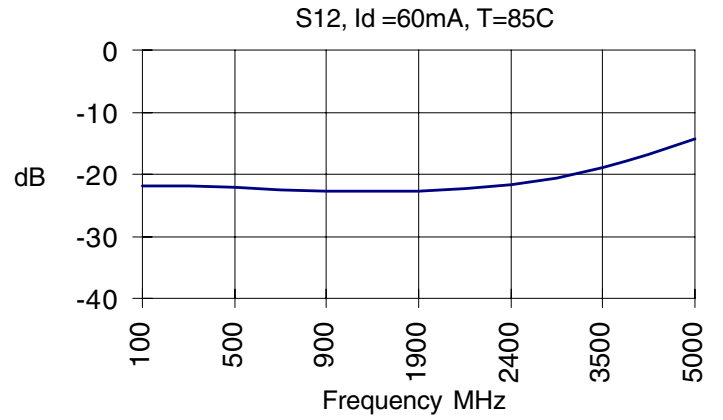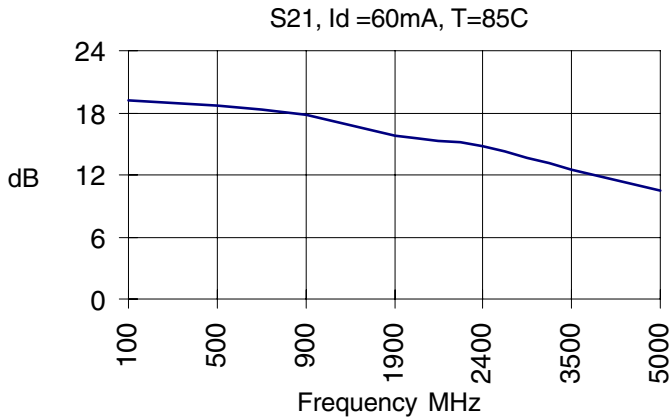

The information provided herein is believed to be reliable at press time. Stanford Microdevices assumes no responsibility for inaccuracies or omissions. Stanford Microdevices assumes no responsibility for the use of this information, and all such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. Stanford Microdevices does not authorize or warrant any Stanford Microdevices product for use in life-support devices and/or systems. Copyright 1999 Stanford Microdevices, Inc. All worldwide rights reserved.

